

Industrial Drives and Applications-BEE702

Module-2

DC Current Motor Drives

Presented By,

Kavyashree S

Assistant Professor

Department of EEE

ATMECE, Mysuru

1


Syllabus

Direct Current Motor Drives:


- Controlled Rectifier Fed dc Drives,
- Single Phase Fully Controlled Rectifier Control of dc Separately Excited Motor,
- Single Phase Half Controlled Rectifier Control of dc Separately Excited Motor,
- Three Phase Fully Controlled Rectifier Control of dc Separately Excited Motor,
- Three Phase Half Controlled Rectifier Control of dc Separately Excited Motor,
- Multiquadrant Operation of dc Separately Excited Motor Fed Form Fully Controlled Rectifier,
- Rectifier Control of dc Series Motor,
- Supply Harmonics,
- Power Factor and Ripple in Motor Current,
- Chopper Control of Separately Excited dc Motor,
- Chopper Control of Series Motor

Controlled Rectifier Fed DC Drives

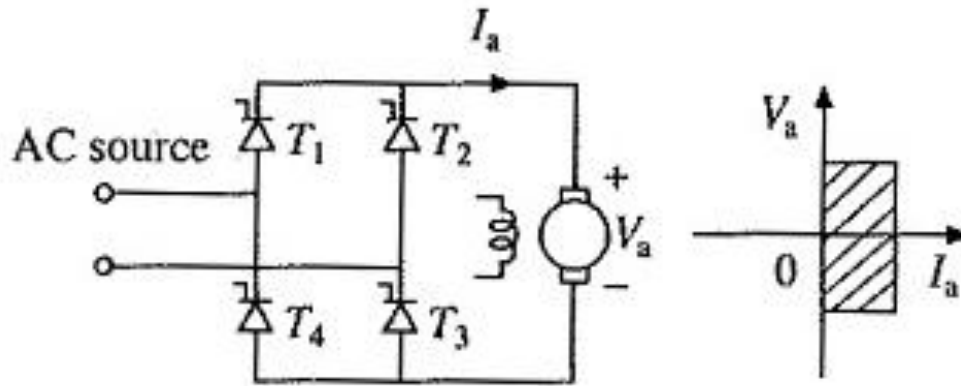
- Controlled Rectifier Fed DC Drives are used to get **variable dc voltage from an ac source of fixed voltage**.
- Controlled Rectifier Fed DC Drives are also known as Static Ward-Leonard drives.



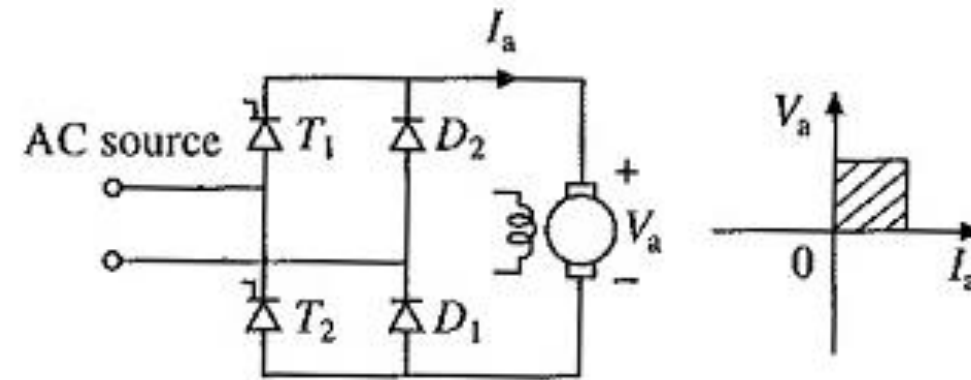
(a) Single-phase fully-controlled rectifier



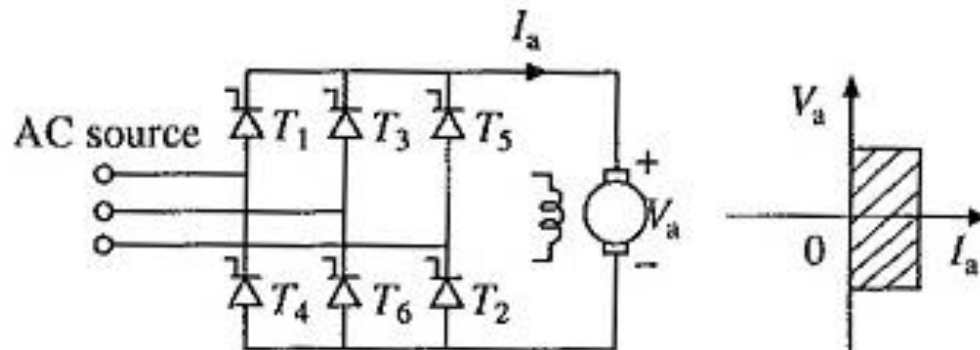(b) Single-phase half-controlled rectifier



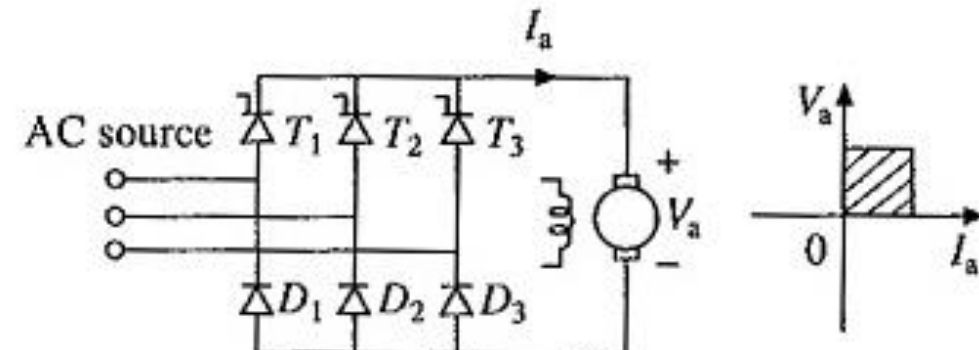
(c) Three-phase fully-controlled rectifier



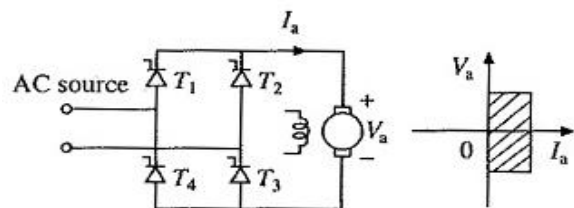
(d) Three-phase half-controlled rectifier

Controlled Rectifier Fed DC Drives cntd.


- Figure shows commonly used **Controlled Rectifier Fed DC Drives** and **quadrants** in which they can **operate on V_a - I_a plane**.
- As **thyristors** are capable of **conducting current only in one direction**, all these rectifiers are capable of providing current only in one direction.
- Rectifiers of **Figs.(a) and (c)** provide **control of dc voltage in either direction** and therefore, allow **motor control in quadrants I and IV**. They are known as **Fully Controlled Rectifiers**.
- Rectifiers of **Figs.(b) and (d)** as they allow **dc voltage control only in one direction** and **motor control in quadrant I only**. They are called **Half Controlled Rectifiers**
- For low power applications (up to around 10 kW) single-phase rectifier drives are employed. For high power applications, three-phase rectifier drives are used. Exception is made in traction where single phase drives are employed for large power ratings.



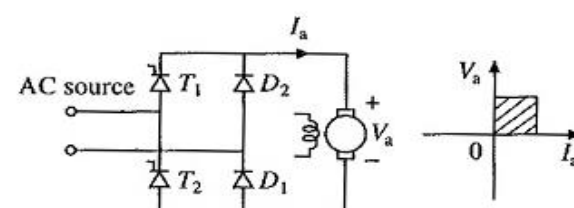
(a) Single-phase fully-controlled rectifier



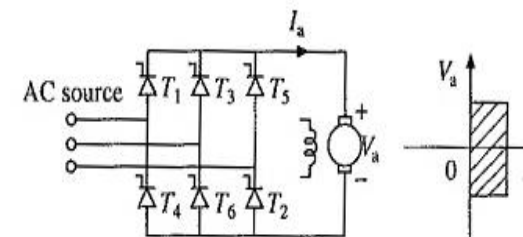(b) Single-phase half-controlled rectifier



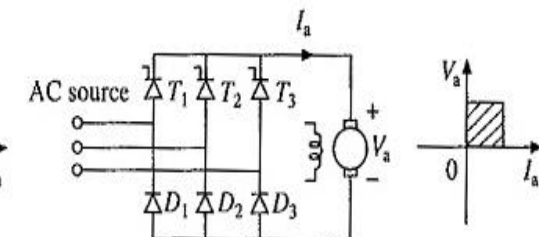
(c) Three-phase fully-controlled rectifier



(d) Three-phase half-controlled rectifier

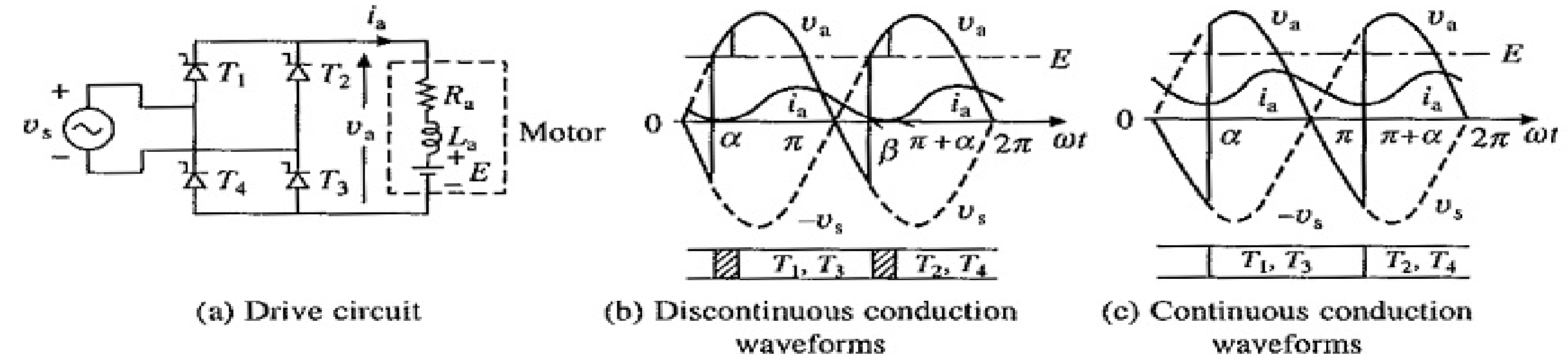1. Single Phase Fully Controlled Rectifier Control of DC Motor


- The Single Phase Fully Controlled Rectifier Control of DC Motor is shown in Fig. (a).




- Motor is shown by its equivalent circuit.
- Field supply is not shown.
- When field control is required, field is fed from a controlled rectifier, otherwise from an uncontrolled rectifier.
- The ac input voltage is defined by

$$v_s = V_m \sin \omega t$$

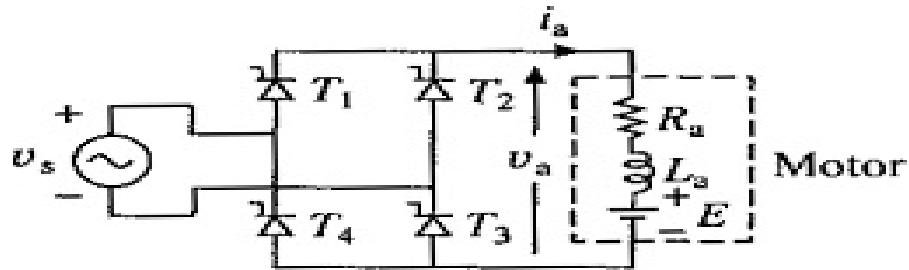
1. Single Phase Fully Controlled Rectifier Control of DC Motor cntd.



(a) Drive circuit

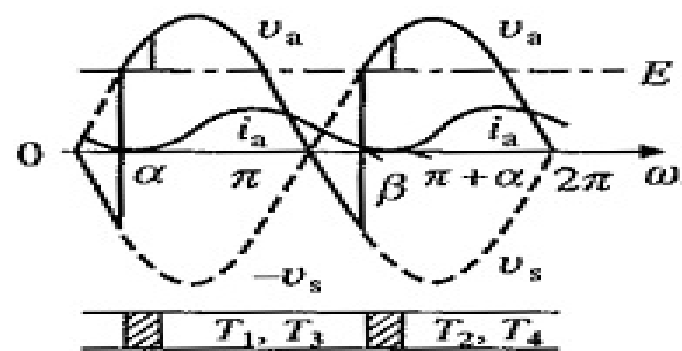

(b) Discontinuous conduction waveforms

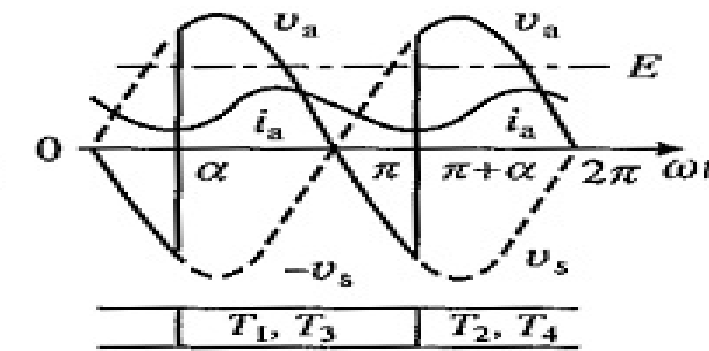


(c) Continuous conduction waveforms

- In a cycle of source voltage, thyristors **T1 and T3** are given **gate signals from α to π** , and thyristors **T2 and T4** are given **gate signals from $(\pi + \alpha)$ to 2π** .
- When armature current does not flow continuously, the motor is said to operate in discontinuous conduction.
- When current flows continuously, the conduction is said to be continuous.
- The drive under consideration, predominantly operates in discontinuous conduction.
- Discontinuous conduction has several modes of operation.

Discontinuous conduction mode


- In discontinuous conduction mode of Single Phase Fully Controlled Rectifier Control of DC Motor, current starts flowing with the turn-on of thyristors **T1** and **T3** at $\omega t = \alpha$.
- Motor gets connected to the source and its terminal voltage equals v_s .
- The current, which flows against both, E and the source voltage after $\omega t = \pi$, falls to zero at β .
- Due to the absence of current, T1 and T3 turn-off. Motor terminal voltage is now equal to its induced voltage E .
- When thyristors T2 and T4 are fired at $(\pi + \alpha)$, next cycle of the motor terminal voltage v_a starts.

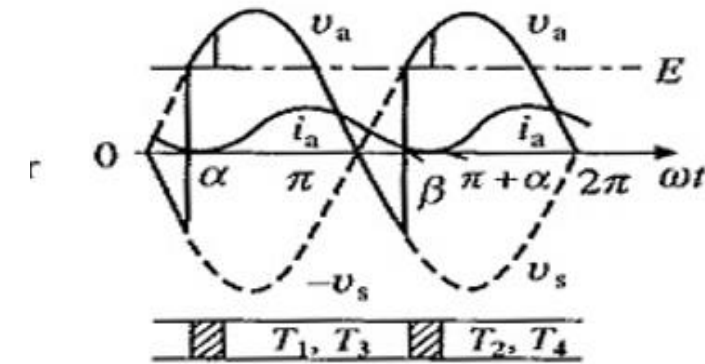

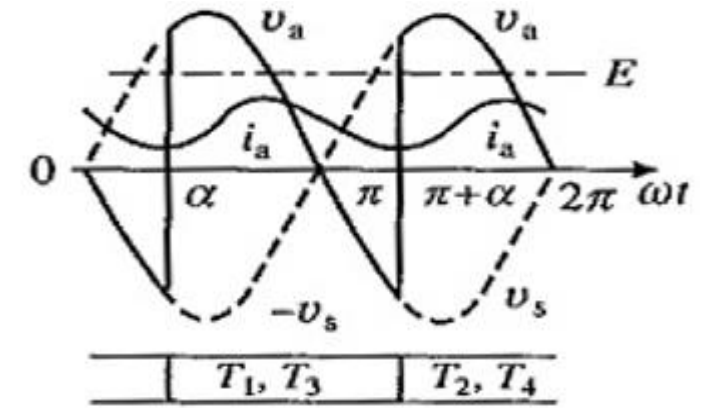(b) Discontinuous conduction waveforms

Continuous conduction mode

- In continuous conduction mode of Single Phase Fully Controlled Rectifier Control of DC Motor, a positive current flows through the motor, and T2 and T4 are in conduction just before α .
- Application of gate pulses turns on forward biased thyristors T1 and T3 at α .
- Conduction of T1 and T3 reverse biases T2 and T4 and turns them off.
- A cycle of v_a is completed when T2 and T4 are turned-on at $(\pi + \alpha)$ causing turn-off of T1 and T3.




(c) Continuous conduction waveforms

Discontinuous Conduction

In a Single Phase Fully Controlled Rectifier Control of DC Motor terminal voltage v_a , the drive operates in two intervals

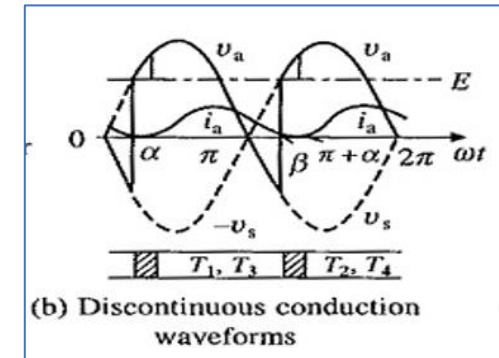- Duty interval ($\alpha \leq \omega t \leq \beta$) when motor is connected to the source and $v_a = v_s$.
- Zero current interval ($\beta \leq \omega t \leq \pi + \alpha$) when $i_a = 0$ and $v_a = E$.



Drive operation is described by the following equations

$$v_a = R_a i_a + L_a \frac{di_a}{dt} + E = V_m \sin \omega t, \text{ for } \alpha \leq \omega t \leq \beta \quad (1)$$

$$v_a = E \quad \text{and} \quad i_a = 0 \quad \text{for} \quad \beta \leq \omega t \leq \pi + \alpha$$

Simplifying eqn (1)

$$i_a(\omega t) = \frac{V_m}{Z} \sin(\omega t - \phi) - \frac{E}{R_a} + K_1 e^{-t/\tau_a} \quad \text{for } \alpha \leq \omega t \leq \beta$$

$$Z = \sqrt{R_a^2 + (\omega L_a)^2}$$

$$\phi = \tan^{-1} (\omega L_a / R_a)$$

$$i_a(\omega t) = \frac{V_m}{Z} [\sin(\omega t - \phi) - \sin(\alpha - \phi)e^{-(\omega t - \alpha) \cot \phi}] - \frac{E}{R_a} [1 - e^{-(\omega t - \alpha) \cot \phi}], \quad \text{for } \alpha \leq \omega t \leq \beta$$

$$\text{As } i_a(\beta)=0 \quad \begin{array}{l} \longrightarrow \\ \longrightarrow \end{array} \frac{V_m}{Z} \sin(\beta - \phi) - \frac{E}{R_a} + \left[\frac{E}{R_a} - \frac{V_m}{Z} \sin(\alpha - \phi) \right] e^{-(\beta - \alpha) \cot \phi} = 0$$

Since voltage drop across the armature inductance due to dc component of armature current is zero

$$V_a = E + I_a R_a$$

where V_a and I_a are respectively dc components of armature voltage and current respectively.

Armature voltage

From Fig (b)

$$\begin{aligned} V_a &= \frac{1}{\pi} \left[\int_{\alpha}^{\beta} V_m \sin \omega t d(\omega t) + \int_{\beta}^{\pi + \alpha} E d(\omega t) \right] \\ &= \frac{V_m (\cos \alpha - \cos \beta) + (\pi + \alpha - \beta) E}{\pi} \end{aligned}$$

Drive operation is described by the following equations

- Armature current consists of dc component I_a and harmonics.
- When flux is constant, only dc component produces steady torque.
- Harmonics produce alternating torque components, the average value of which is zero.

Therefore, **Speed is given by**

$$\omega_m = \frac{V_m (\cos \alpha - \cos \beta)}{K(\beta - \alpha)} - \frac{\pi R_a}{K^2 (\beta - \alpha)} T$$

- Boundary between continuous and discontinuous conduction is reached when $\beta = \pi + \alpha$.

Substituting $\beta = \pi + \alpha$ in Eq. **Critical value of speed is given by,**

$$\omega_{mc} = \frac{R_a V_m}{ZK} \sin (\alpha - \phi) \left[\frac{1 + e^{-\pi \cos \phi}}{e^{-\pi \cos \phi} - 1} \right]$$

Armature voltage

$$V_a = \frac{1}{\pi} \int_{\alpha}^{\pi+\alpha} V_m \sin \omega t d(\omega t) = \frac{2V_m}{\pi} \cos \alpha$$

Speed



$$\omega_m = \frac{2V_m}{\pi K} \cos \alpha - \frac{R_a}{K^2} T$$

- Speed torque curves for the drive are shown in Fig.
- The ideal no load operation is obtained when $I_a = 0$.
- When both thyristor pairs (T_1, T_3) and (T_2, T_4) fail to fire, I_a will be zero.
- This will happen when $E > v_s$ throughout the period for which firing pulses are present.
- Therefore, when $\alpha < \pi/2$, E should be greater or equal to V_m and when $\alpha > \pi/2$, E should be greater or equal to $V_m \sin \omega t$.
- Therefore, **no load speeds** are given by


$$\begin{aligned} \omega_{m0} &= \frac{V_m}{K}, \quad \text{for } 0 \leq \alpha \leq \pi/2 \\ &= \frac{V_m \sin \alpha}{K}, \quad \text{for } \pi/2 \leq \alpha \leq \pi \end{aligned}$$

Continuous Conduction


- Maximum average terminal voltage ($2V_m/\pi$) is chosen equal to the rated motor voltage.
- Ideal no load speed of the motor when fed by a perfect direct voltage of rated value will then be ($2V_m/\pi K$).
- It is interesting to note that the maximum no load speed with rectifier control is $(\pi/2)$ times this value.
- Boundary between continuous and discontinuous conduction is shown by dotted line.
- For torques less than rated, a low power drive mainly operates in discontinuous conduction.

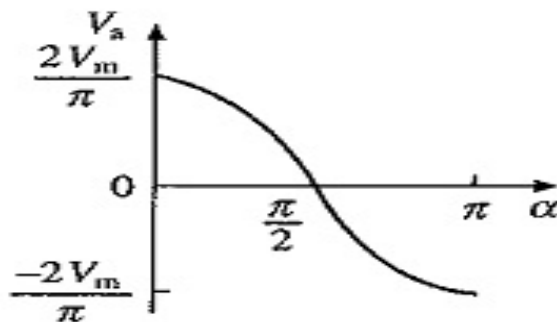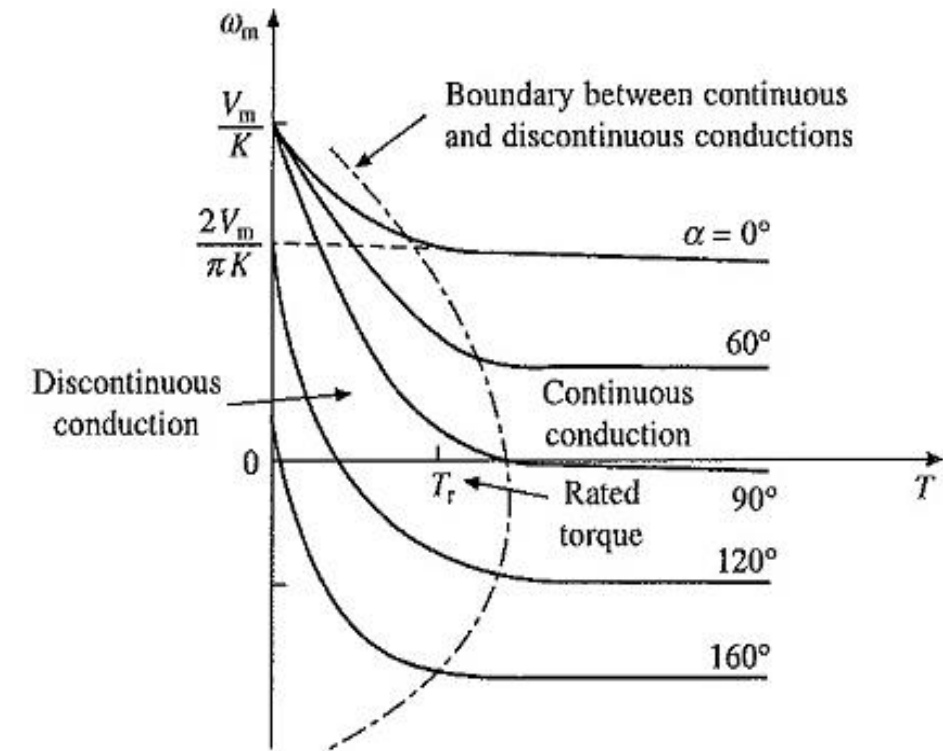

(a) $V_a - \alpha$ curve

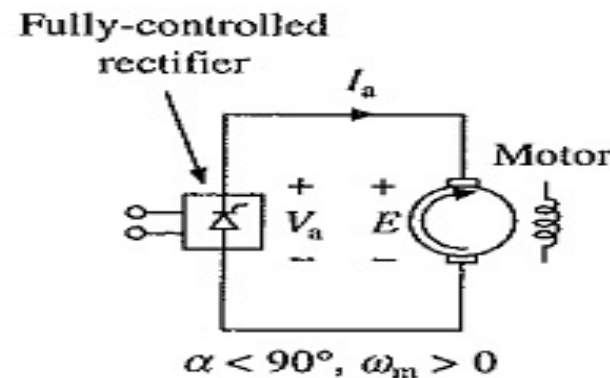


(b) Motoring

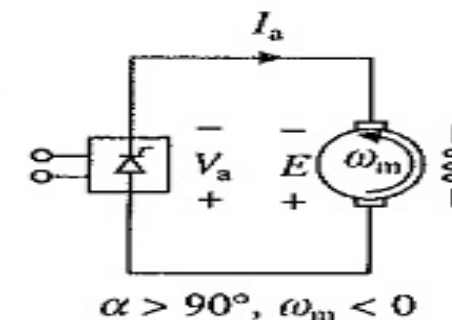


(c) Regenerative braking

- Two quadrant operation capability of the drive can be utilized only with overhauling loads or other active loads which can drive the motor in reverse direction.
- In a normal two quadrant operation of a motor one needs forward motoring (quadrant I) and forward braking (quadrant II) which cannot be provided by the drive

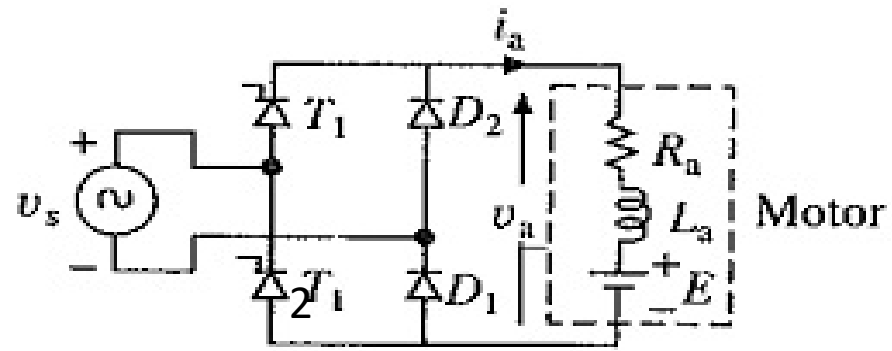
2. Single Phase Half Controlled Rectifier Control of DC Separately Excited Motor



(a) Drive circuit

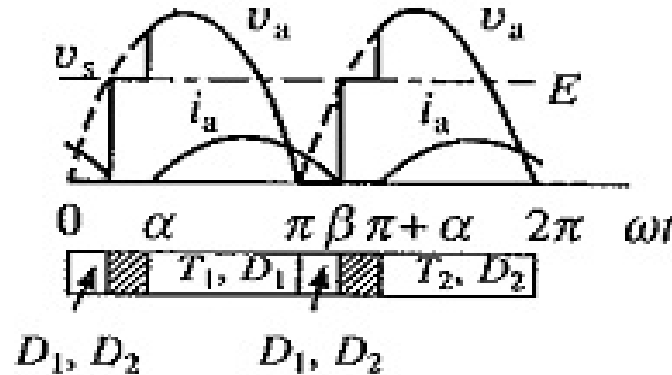


(b) Discontinuous conduction waveforms

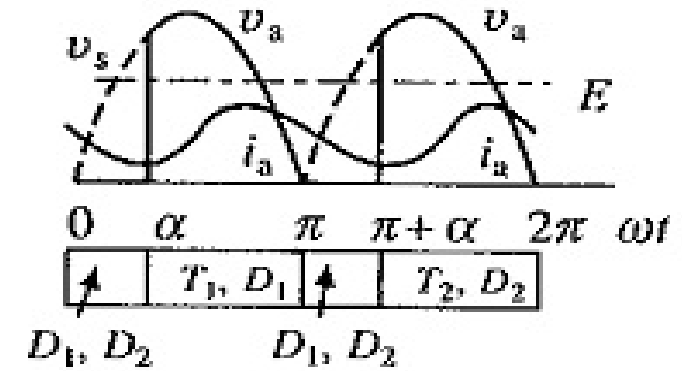


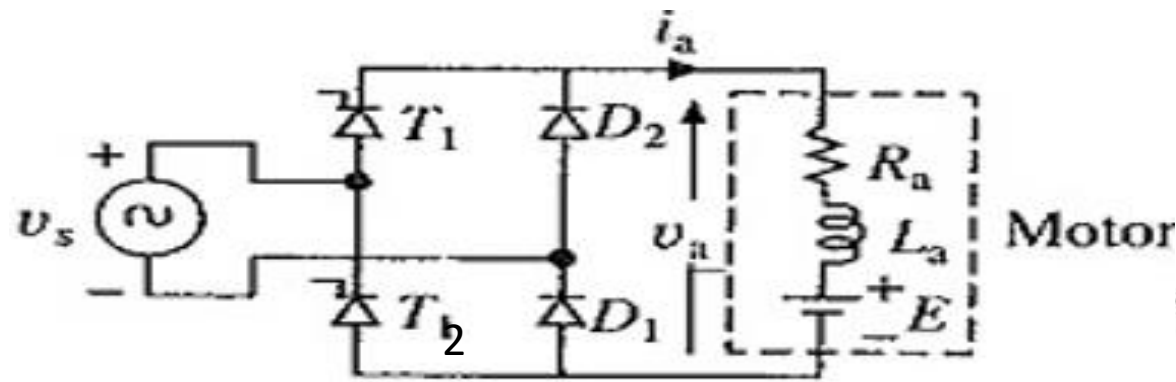(c) Continuous conduction waveforms

- Single Phase Half Controlled Rectifier Control is shown in Fig.
- T_1 receives **gate pulse** from α to π and T_2 from $(\pi + \alpha)$ to 2π . Motor terminal voltage and current waveforms for the dominant discontinuous and continuous conduction mode are shown above




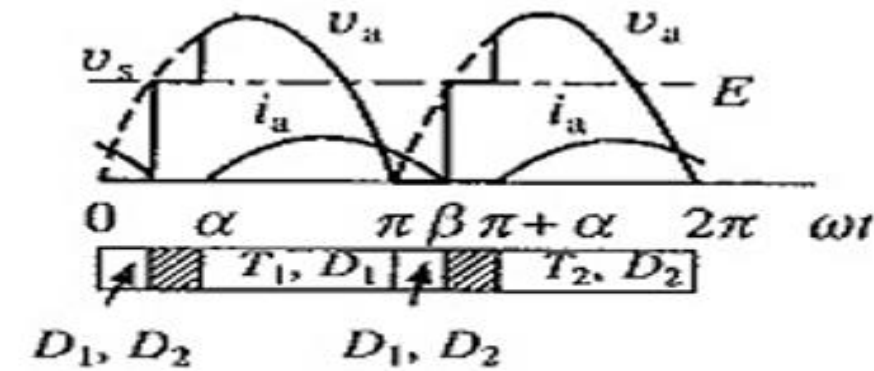- In **discontinuous conduction mode**, when **T1 is fired at α** , motor gets connected to the source through T1 and D1 and **$v_a = v_s$** .



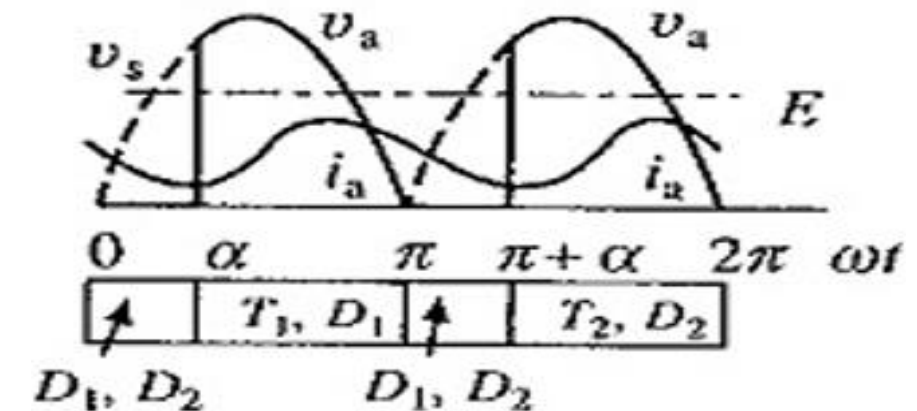(b) Discontinuous conduction waveforms

- The armature current flows and **D2 gets forward biased at π** .
- Consequently, **armature current freewheels** through the path formed by **D1 and D2**, and the **motor terminal voltage is zero**.
- Conduction of **D2 reverse biases T1 and turns it off**.
- **Armature current drops to 0 at β and stays zero until T2 is fired at $(\pi + \alpha)$** . Similarly, the continuous conduction mode can be explained.



(c) Continuous conduction waveforms

Discontinuous Conduction

i. Duty interval ($\alpha \leq \omega t \leq \pi$): Substitution of $\omega t = \pi$ in Armature current equation gives $i_a(\pi)$.

ii. Freewheeling interval ($\pi \leq \omega t \leq \beta$): Operation is governed by the following equation:

$$i_a R_a + L_a \frac{di_a}{dt} + E = 0$$

$$i_a(\omega t) = \frac{V_m}{Z} [\sin \phi \cdot e^{-(\omega t - \pi) \cot \phi} - \sin(\alpha - \phi) \cdot e^{-(\omega t - \alpha) \cot \phi}] - \frac{E}{R_a} [1 - e^{-(\omega t - \alpha) \cot \phi}], \quad \text{for } \pi \leq \omega t \leq \beta$$


iii. Zero current interval ($\beta \leq \omega t \leq \pi + \alpha$): Equation (5.73) is applicable. Since $i_a(\beta) = 0$, one gets from

$$e^{\beta \cot \phi} = \frac{R_a V_m}{Z E} [\sin \phi e^{\pi \cot \phi} - \sin(\alpha - \phi) e^{\alpha \cot \phi}] + e^{\alpha \cot \phi}$$

$$V_a = \frac{1}{\pi} \left[\int_{\alpha}^{\pi} V_m \sin \omega t d(\omega t) + \int_{\beta}^{\pi + \alpha} E d(\omega t) \right]$$

$$= \frac{V_m (1 + \cos \alpha) + (\pi + \alpha - \beta) E}{\pi}$$
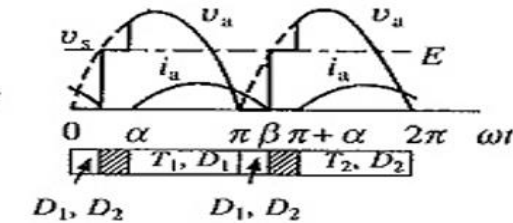
$$\omega_m = \frac{V_m (1 + \cos \alpha)}{K(\beta - \alpha)} - \frac{\pi R_a}{K^2 (\beta - \alpha)} T$$




(b) Discontinuous conduction waveforms

Continuous Conduction

$$V_a = \frac{1}{\pi} \int_{\alpha}^{\pi} V_m \sin \omega t d(\omega t) = \frac{V_m}{\pi} (1 + \cos \alpha)$$

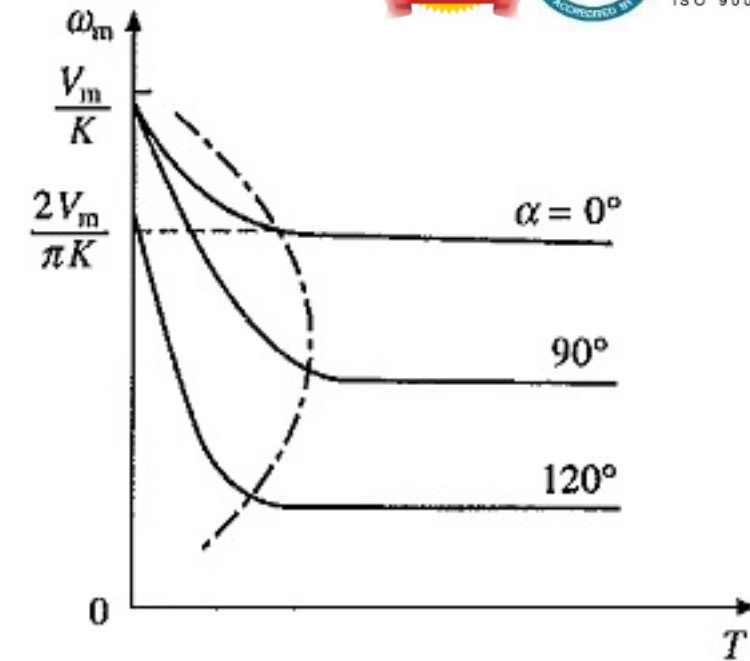
$$\omega_m = \frac{V_m}{\pi K} (1 + \cos \alpha) - \frac{R_a}{K^2} T$$




- The output voltage cannot be reversed.
- When coupled to an active load, in the motor speed can reverse, reversing E as shown in Fig. (b).
- As current direction does not change, machine now works as a generator producing braking torque.
- Since, rectifier voltage cannot reverse, generated energy cannot be transferred to ac source, and therefore, it is absorbed in the armature circuit resistance.

- **Braking** so obtained is nothing but the **reverse voltage braking (plugging)**.
- Such a braking is not only inefficient, but also causes a large current [$I_a = (V_a + E)/R_a$] to flow through the rectifier and motor.
- Since it cannot be regulated by adjustment of firing angle, it will damage the rectifier and motor.
- Therefore, when load is active, care should be taken to avoid such a operation. If such a operation cannot be avoided, fully-controlled rectifier should be used.

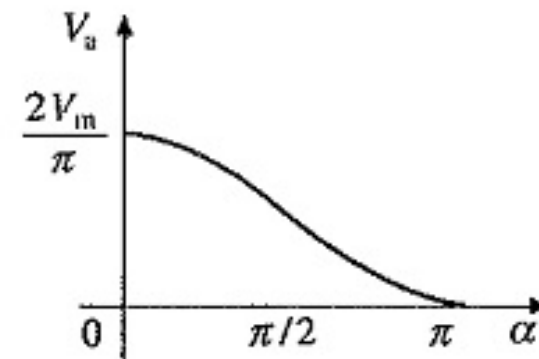A Single Phase Half Controlled Rectifier Control is cheaper and gives higher power factor compared to single-phase fully-controlled rectifier. But then it only provides control in quadrant I.




(a) $V_a - \alpha$ curve

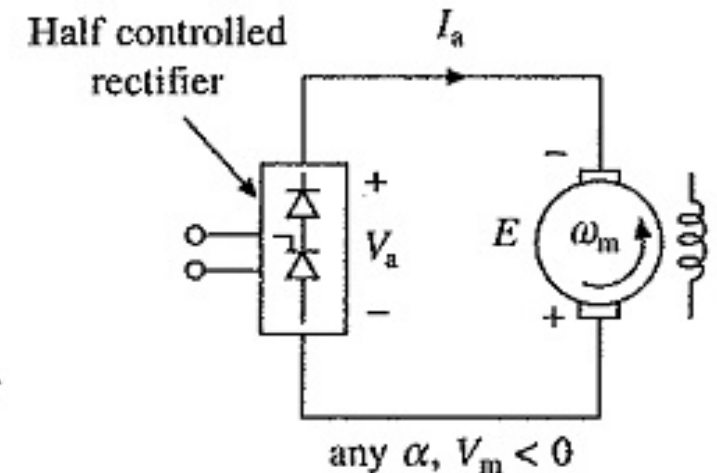


(b) Braking operation

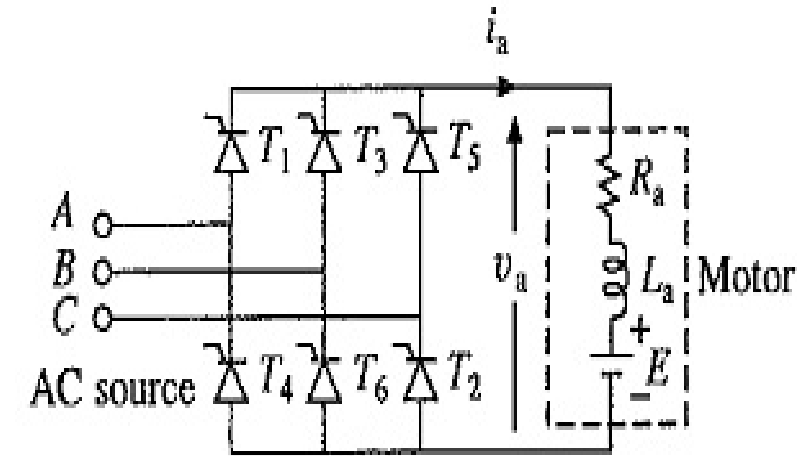3. Three phase Fully Controlled Rectifier Control of DC Separately Excited Motor


- Three phase Fully Controlled Rectifier Control (6 pulse) fed separately excited dc motor drive is shown in Fig. (a).
- Thyristors are fired in the sequence of their numbers with a phase difference of 60° by gate pulses of 120° duration.
- Each thyristor conducts for 120° , and two thyristors conduct at a time—one from upper group (odd numbered thyristors) and the other from lower group (even numbered thyristors) applying respective line voltage to the motor.



(a) Drive circuit

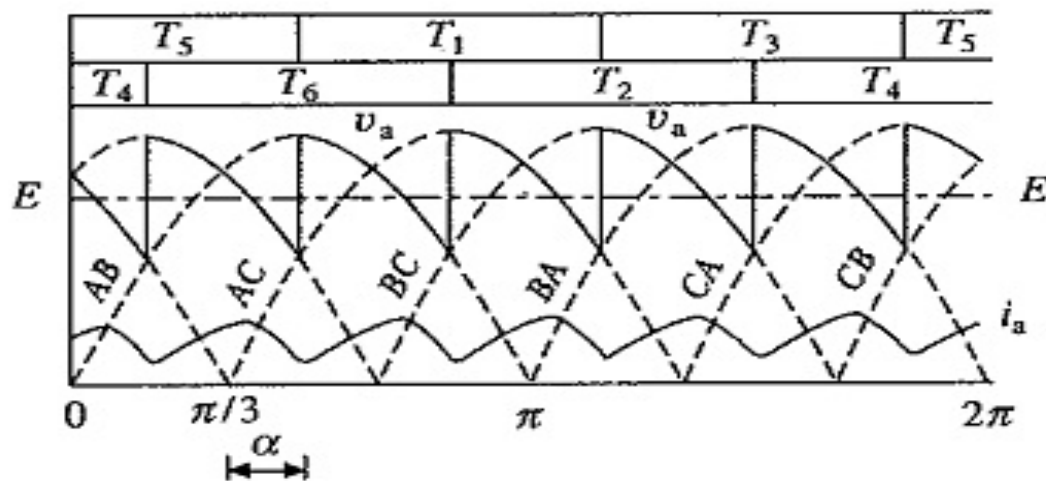

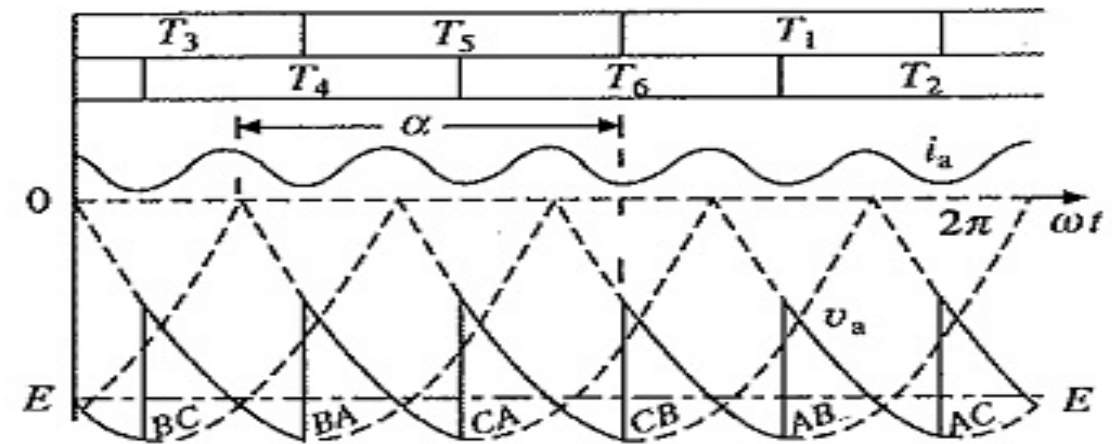(b) Motoring operation, $\alpha = 30^\circ$




(c) Braking operation $\alpha \approx 140^\circ$


60° A Phase: A- T1 - M – T6 – B
A- T1 – M- T2- C

60° B Phase: B- T3 - M – T2 – C
B- T3 – M- T4- A

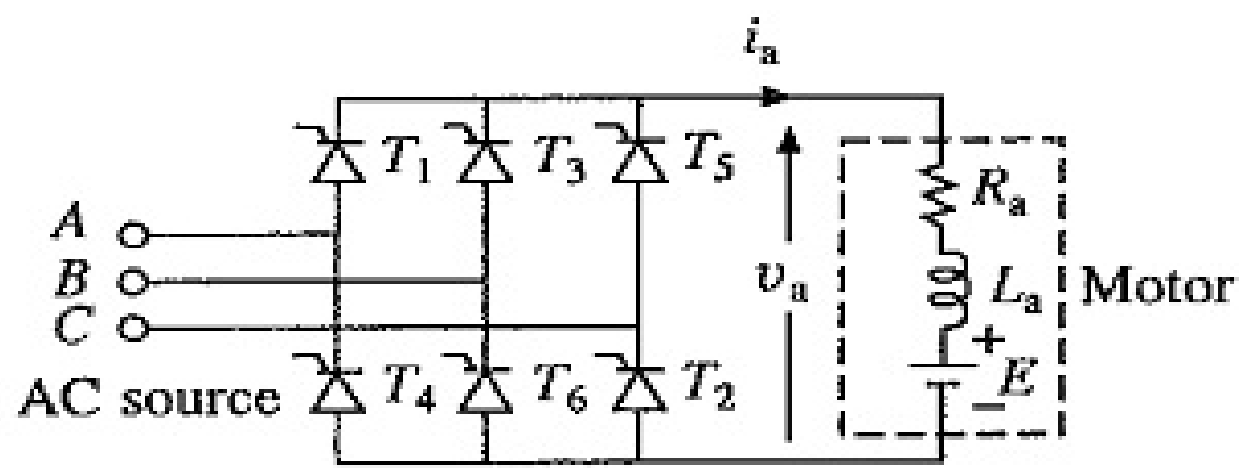60° C Phase: C- T5 - M – T4 – A
C- T5 – M- T6- B




(a) Drive circuit

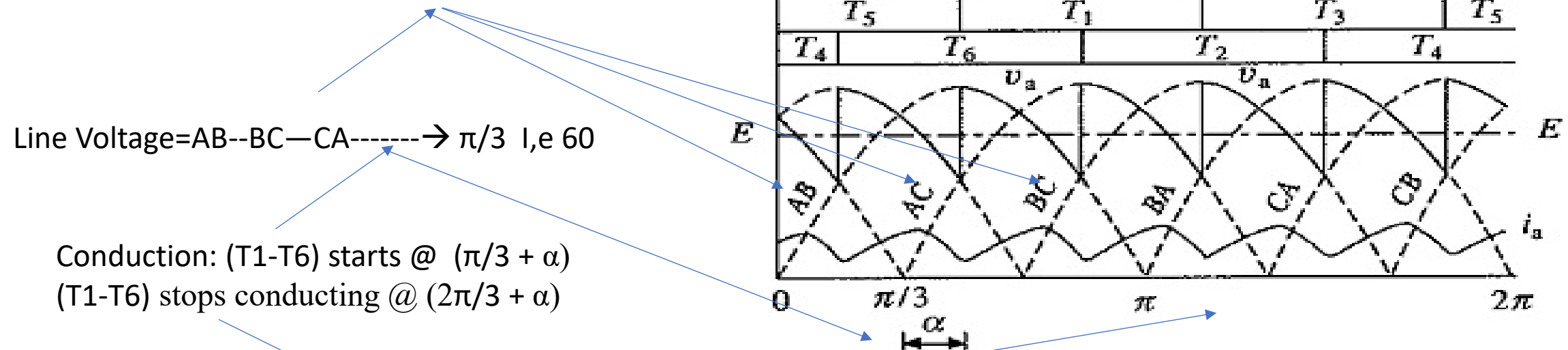

(b) Motoring operation, $\alpha = 30^\circ$

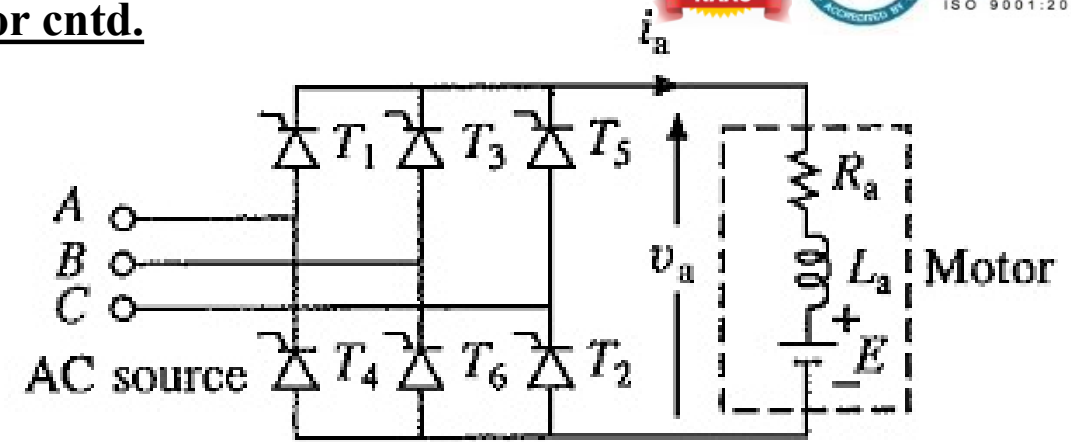
3. Three phase Fully Controlled Rectifier Control of DC Separately Excited Motor cntd.

- Transfer of current from an outgoing to incoming thyristor can take place when the respective line voltage is of such a polarity that not only it forward biases the incoming thyristor, but also leads to the reverse biasing of the outgoing when incoming turns-on.



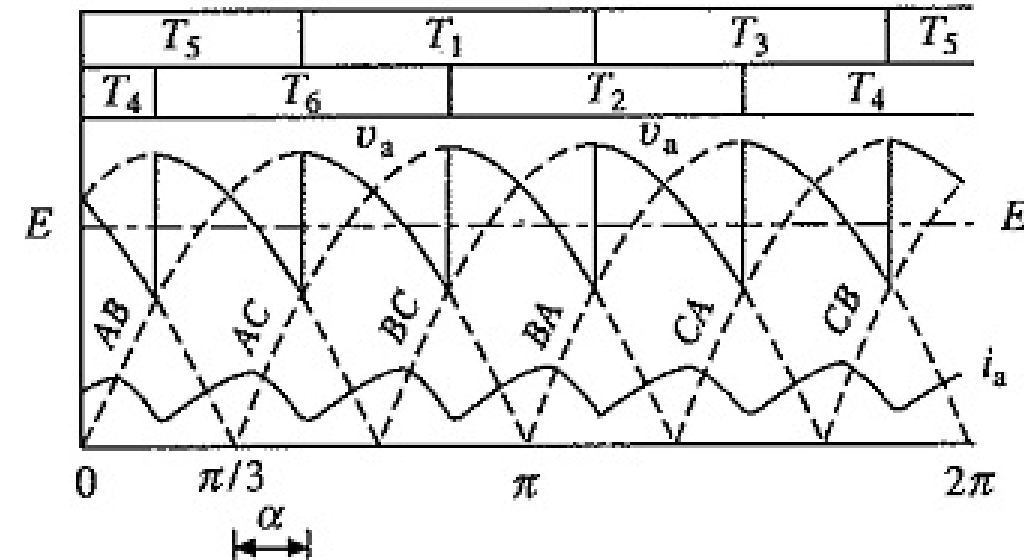(a) Drive circuit

- Thus, firing angle for a thyristor is measured from the instant when the respective line voltage is zero and increasing.
- For example, the transfer of current from thyristor T_5 to thyristor T_1 can occur as long as the line voltage v_{AC} is positive.
- Hence, for thyristor T_1 , firing angle α is measured from the instant $v_{AC} = 0$ and increases.



(b) Motoring operation, $\alpha = 30^\circ$

3. Three phase Fully Controlled Rectifier Control of DC Separately

Excited Motor cntd.

$$v_{AB} = V_m \sin \omega t$$

$$\alpha = \omega t - \pi/3$$

- If line voltage v_{AB} is taken as the reference voltage, then
- Motor terminal voltage and current waveforms for continuous conduction are shown in Figs. (b) and (c) for motoring and braking operations, respectively.
- Devices under conduction are also shown in the figure.
- The discontinuous conduction is neglected here because it occurs in a narrow region of its operation.
- For the motor terminal voltage cycle from $\pi/3 + \alpha$ to $2\pi/3 + \alpha$ (from Figs. (b) and (c)).


$$V_a = \frac{3}{\pi} \int_{\alpha + \pi/3}^{\alpha + 2\pi/3} V_m \sin \omega t d(\omega t)$$

$$= \frac{3}{\pi} V_m \cos \alpha$$

$$\omega_m = \frac{3V_m}{\pi K} \cos \alpha - \frac{R_a}{K^2} T$$

Prepared by Kavyashree S, Asst Prof, EEE

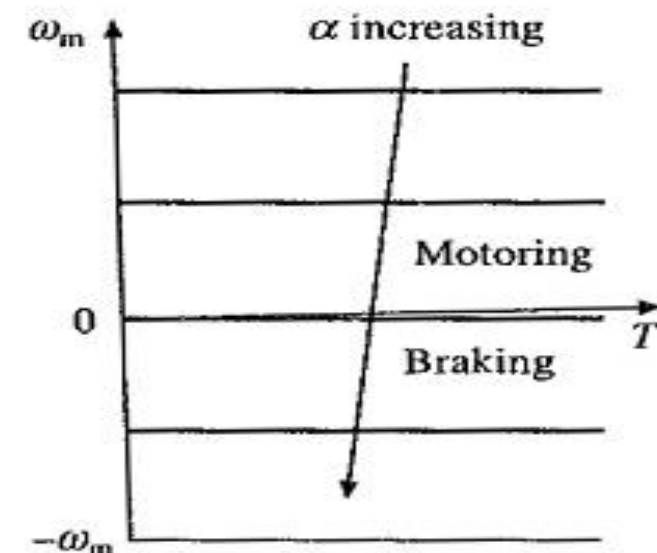- When discontinuous conduction is ignored, speed-torque curves of Fig. are obtained.
- The V_a vs α curve has same nature as shown in Fig. (a) for single-phase case.
- Consequently, drive operates in quadrants I and IV.




4. Three Phase Half Controlled Rectifier Control of DC Separately Excited Motor

- For rectifier circuit, shown in Fig. (d), under continuous conduction


$$V_a = \frac{3V_m}{2\pi} (1 + \cos \alpha)$$
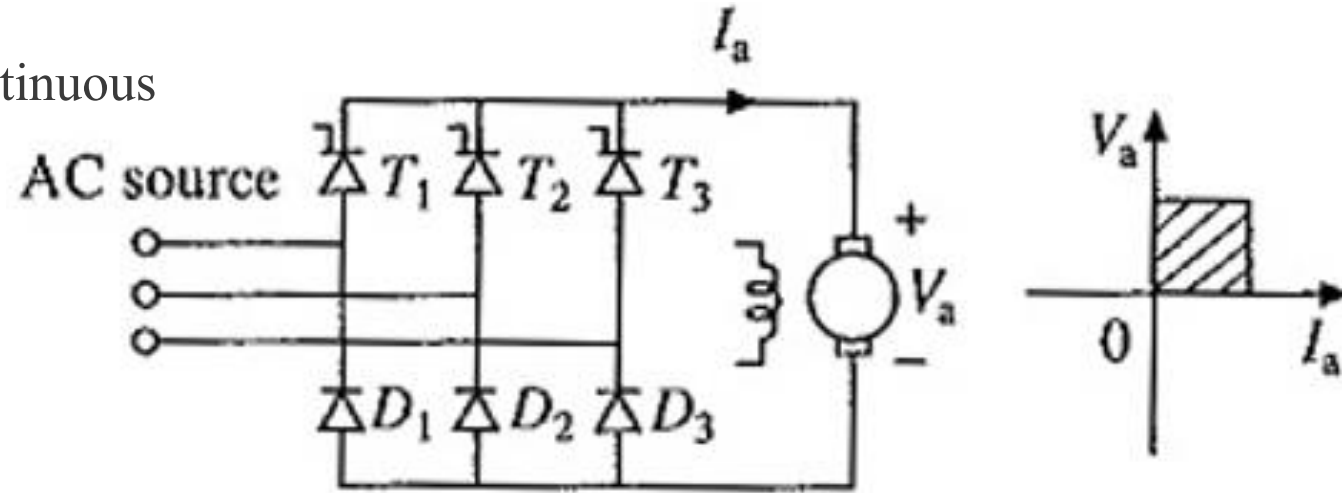
$$\omega_m = \frac{3V_m}{2\pi K} (1 + \cos \alpha) - \frac{R_a}{K^2} T$$



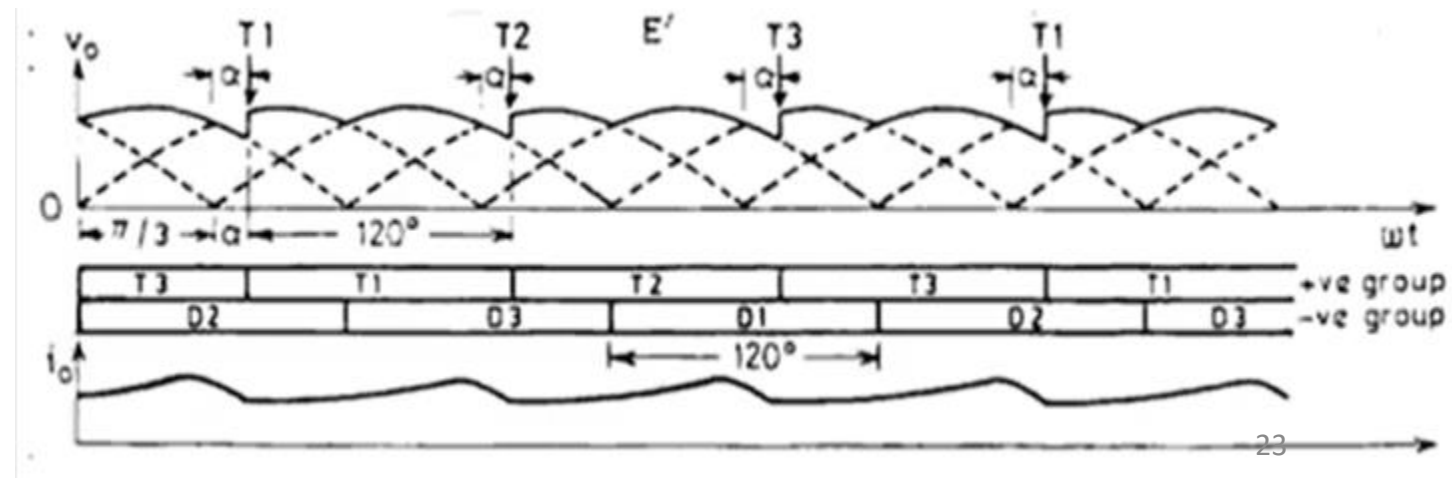(d) Three-phase half-controlled rectifier

V_a vs α curve has same nature as shown in Fig.(a). Consequently, drive operates only in quadrant I.



5. Multi-quadrant Operation of dc Separately Excited Motor Fed From Fully Controlled Rectifier

1. DC Motor Reversing Switch Diagram
2. Dual Converter Control of DC Separately Excited Motor
3. Four Quadrant Drive With Field Reversal

https://www.youtube.com/watch?v=wa_shoXzcmg

5. Multi-quadrant Operation of dc Separately Excited Motor Fed Form Fully Controlled Rectifier cntd.

1. DC Motor Reversing Switch Diagram

a. **DC Motor Reversing Switch Diagram** is shown in Fig. (a).

- A fully-controlled rectifier feeds the motor through a reversing switch RS, a mechanical reversing switch, which is used to reverse the armature connection with respect to the rectifier.
- A fully-controlled rectifier: i_a flows from A1 to A2 - capable of providing operation in **quadrants I** (Forward Motoring) and **IV** (Reverse Regenerative Braking).
- The reversal of the armature connection: i_a flows from A2 to A1 provides operation in **quadrant III** (Reverse Motoring) and **II** (Forward Regenerative Braking).

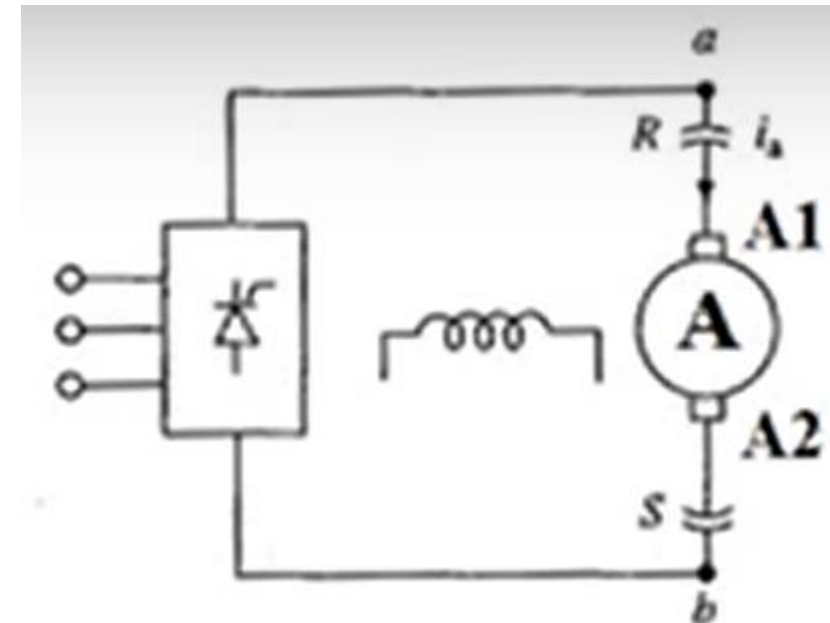



Fig. (a): DC Motor Reversing Switch Diagram.

1. DC Motor Reversing Switch Diagram

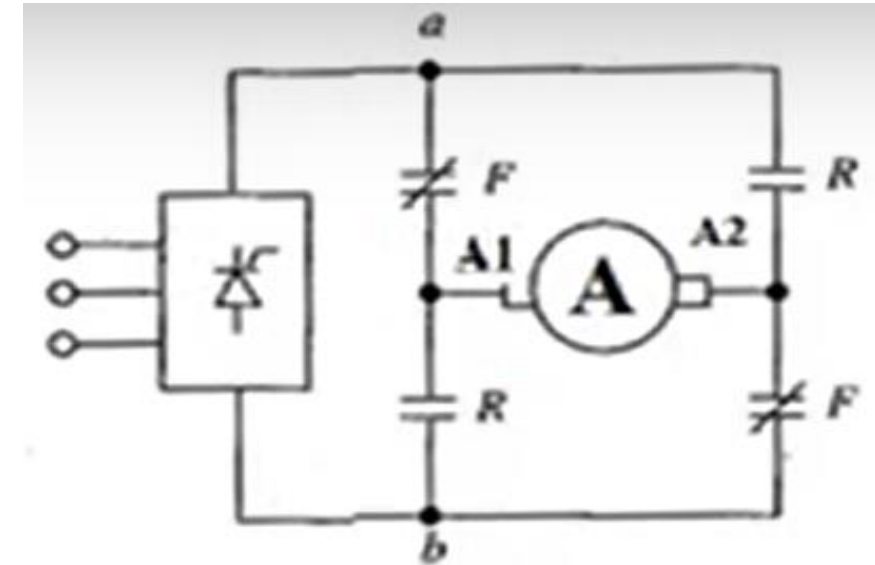b) DC Motor Reversing Switch with relay-operated contactor

The DC Motor Reversing Switch Diagram consisting a relay-operated contactor with two contacts- normally open and two normally closed as shown in Fig. (b).

- F contactor Closed- i_a flows from A1 to A2, operating in Quadrants I and IV.
- R contactor Closed- i_a flows from A2 to A1, operating in Quadrants III and II.




b) DC Motor Reversing Switch with relay-operated contactor

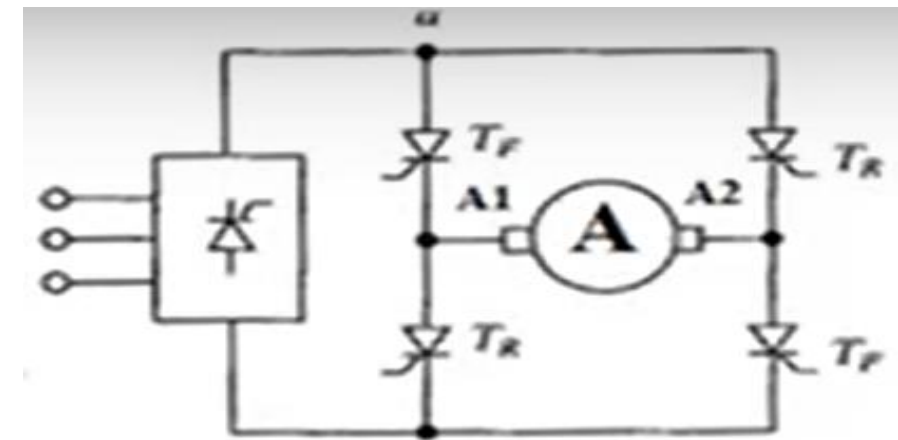c) DC Motor Reversing Switch with Thyristor

When slow operation and frequent maintenance associated with the contactor is not acceptable, reversing switch is realized using four thyristors as shown in Fig. (c).

- With thyristor pair T_F closed: i_a flows from A1 to A2, operating in Quadrants I and IV.
- With thyristor pair T_R closed: i_a flows from A2 to A1, operating in Quadrants III and II.



c) DC Motor Reversing Switch with Thyristor

- In both the configurations of RS, the switching is done at zero current in order to avoid voltage spikes and to reduce its rating.
- The speed reversal (transfer of operation from quadrant I to III or from quadrant III to I) is done as follows:
- The firing angle of the rectifier is set at the highest value. It works as an inverter and reduces armature current to zero.
- After the zero current is sensed, firing pulses are stopped.
- A delay time of 2 to 10 ms is provided to make sure that the thyristors which were conducting have all fully turned off.
- Such long delay (compared to thyristor turn-off time which is of few hundred microseconds) is required in order to take care of errors in zero current sensing.
- Now the armature connection is reversed and firing pulses are released with the firing angle set at the highest value.
- The current control adjust the firing angle continuously so as to brake the motor at the maximum allowable current from initial speed to zero speed and then accelerates the motor (again at the maximum allowable current) to the desired speed in the reverse direction.


The operation at the maximum current during speed reversal ensures braking and acceleration at the maximum motor torque ensuring fast reversal.

2. Dual Converter Control of DC Separately Excited Motor

- **Dual Converter** Control of DC Separately Excited Motor consists of **two fully-controlled rectifiers** connected in **anti-parallel across the armature**.
- For power ratings upto around **10 kW**, **single-phase fully-controlled rectifiers** can be used.
- For **higher ratings**, **three-phase fully controlled rectifiers** are employed.
- **Rectifier A**, which provides **positive motor current and voltage** in either direction, allows motor control in quadrants I and IV
- **Rectifier B** provides motor control in **quadrants III and II**, because it gives **negative motor current and voltage** in either direction

There are two methods of control for the Dual Converter Control of DC Separately Excited Motor:

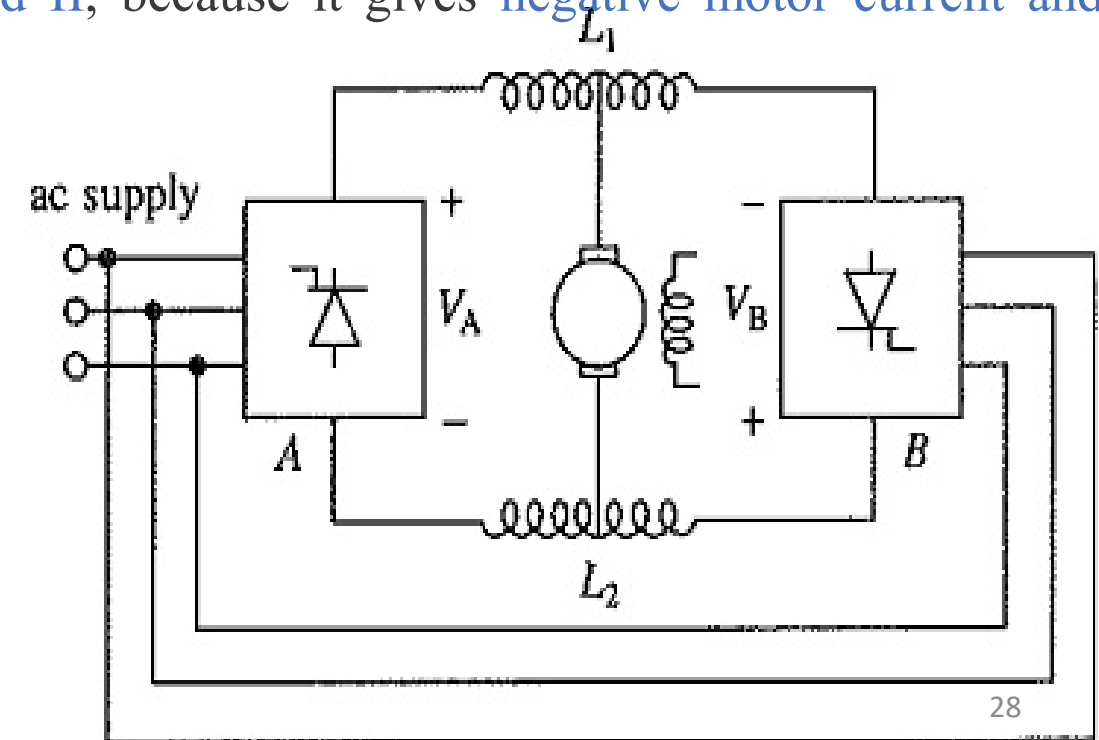- In **simultaneous control** both the rectifiers are controlled together. In order to avoid dc circulating current between rectifiers, they are operated to produce same dc voltage across the motor terminals.
- In **non-simultaneous** or non-circulating current control method, one rectifier is controlled at a time.



a. Simultaneous control

- Both the rectifiers are controlled together
- Although, control of firing angle according to relation prevents dc circulating current, ac current does circulate due to difference between instantaneous output voltages of the two rectifiers. Inductors L_1 and L_2 are added to reduce ac circulating current.
- Because of the flow of ac circulating current, simultaneous control is also known as circulating current control. In a three-phase dual converter, inductors are chosen to allow a circulating current of 30% of full load current.

$$\text{Rectifier A: } V_a = \frac{3V_m}{\pi} \cos \alpha_A = V_A$$

$$\text{Rectifier B: } V_a = \frac{3V_m}{\pi} \cos \alpha_B = V_B$$

$$V_A + V_B = 0$$

$$\frac{3V_m}{\pi} \cos \alpha_A + \frac{3V_m}{\pi} \cos \alpha_B = 0$$

$$\cos \alpha_A + \cos \alpha_B = 0$$

$$\alpha_A + \alpha_B = 180^\circ$$

- This completely **eliminates discontinuous conduction**, and therefore, gives good speed regulation in the complete range of the drive.

2. Dual Converter Control of DC Separately Excited Motor

In Quadrant-I

A- Rectifier Mode : ($0 < \alpha_A < 90^\circ$)


B- Inverter Mode: ($90^\circ < \alpha_B < 180^\circ$)

The speed reversal is done as follows

- For **speed reversal α_A is increased and α_B is decreased** to satisfy the eq $\alpha_A + \alpha_B = 180^\circ$
- The motor back emf exceeds magnitudes of V_A and V_B .
- The **armature current shifts to rectifier B** and the motor operate in **quadrant II**.
- The current control loop adjusts the firing angle α_B continuously so as **to brake the motor** at the maximum allowable current from initial speed to zero speed and then accelerates to the desired speed in the **reverse direction**.

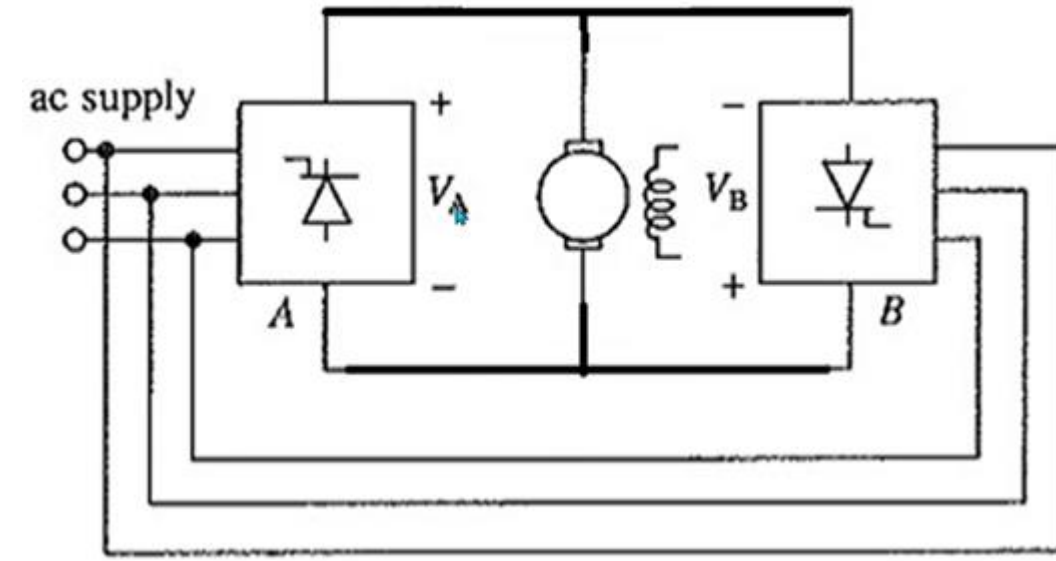b. Non-simultaneous or non-circulating current control method


- One rectifier is controlled at a time.
- When operating in **quadrant I**, **rectifier A** will be **supplying the motor** and **rectifier B** will not be operating.
- The **firing angle of rectifier A** is set at the **highest value**- the rectifier works as an **inverter** and forces the **armature current to zero**.



- After zero current is sensed, a **dead time** of 2 to 10 ms is provided to ensure the **turn-off of all thyristors of rectifier A**.
- Now firing pulses are withdrawn from rectifier A and **transferred to rectifier B**.
- The firing angle rectifier B i.e α_B is set initially at the highest value.
- Now onwards the **current control loop** adjust the firing angle α_B continuously so as to **brake the motor** at the maximum allowable current from initial speed to zero speed and then accelerates to the desired speed in the **reverse direction**

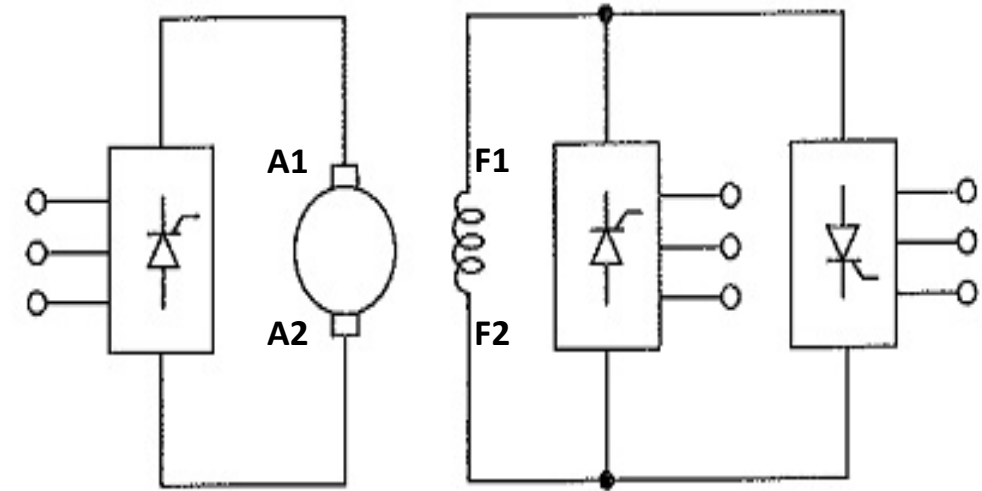3. Field Current Reversal


- Four Quadrant Drive With Field Reversal as shown in Fig, armature is fed from a fully-controlled rectifier and the field from a dual converter so that field current can be reversed.
- With field current in one direction (i_f flows from $F1$ to $F2$), the motor operates in **quadrants I and IV**. When field current is reversed (i_f flows from $F2$ to $F1$), it operates in **quadrants III and II**. The dual converter operates with non-simultaneous control.




The speed reversal is done as follows.

- The **armature rectifier firing angle** is set at the **highest value** to force the **armature current to zero** and then firing pulses are withdrawn.
- The **firing angle** of the **rectifier** supplying the **field** is now set at the **highest value**.
- It **operates as an inverter** and the **field current is forced to zero**.
- After a suitable **dead time**, the **second rectifier** is activated at the **lowest firing angle**.
- When the **field current** has nearly **settled** and the **motor back emf has reversed**, the **firing pulses** of the **armature rectifier** are **released** so as to set the **firing angle at the highest value**.

6. Rectifier Control of DC Series Motor

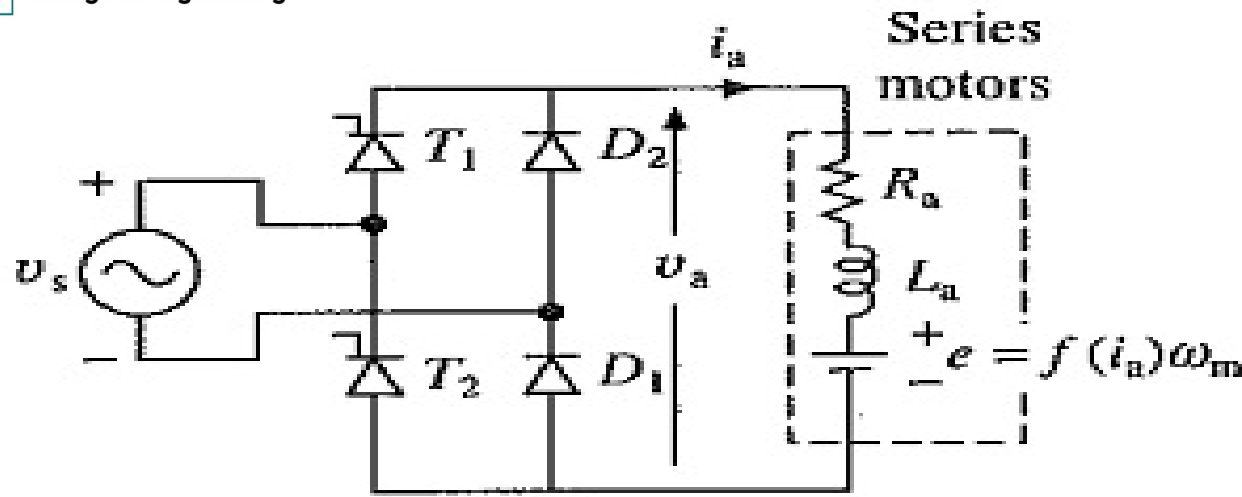

(a) Drive circuit

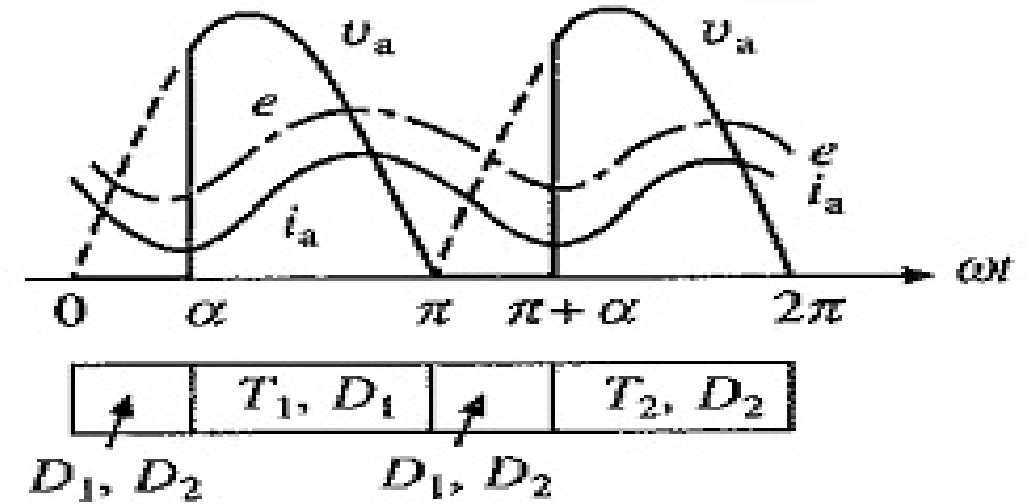

(b) Waveforms

- Single-phase controlled Rectifier Control of DC Series Motor are employed in traction.
- A single-phase half-controlled Rectifier Control of DC Series Motor is shown in Fig. (a). **Equivalent circuit** of motor is also shown.
- Since back emf decreases with armature current, **discontinuous conduction** occurs only in a narrow range of operation.
- The **waveforms** of v_a , i_a and instantaneous back emf e for continuous conduction are shown in Fig. (b).
- Although, in steady state, fluctuations in speed are negligible, **e is not constant but fluctuates with i_a** . For a given speed, e is related to i_a through magnetization curve of motor, which is nonlinear owing to saturation

- Motor operation is described by following equations for duty and freewheeling intervals respectively,

$$V_m \sin \omega t = R_a i_a + L_a \frac{di_a}{dt} + f(i_a) \omega_m, \quad \text{for } \alpha \leq \omega t \leq \pi$$

$$0 = R_a i_a + L_a \frac{di_a}{dt} + f(i_a) \omega_m, \quad \text{for } \pi \leq \omega t \leq (\pi + \alpha)$$

- Because of the presence of term $f(i_a)$, above eqns are nonlinear differential equations and can only be solved numerically. A simple method of analysis is obtained when e is replaced by its average value

$$E_a = K_a \omega_m$$

$$K_a = f(I_a)$$


- Since the drop across the inductance L_a due to dc component of armature current I_a is zero

$$V_a = E_a + I_a R_a$$

$$\omega_m = \frac{V_a - I_a R_a}{K_a}$$


$$T = K_a I_a$$

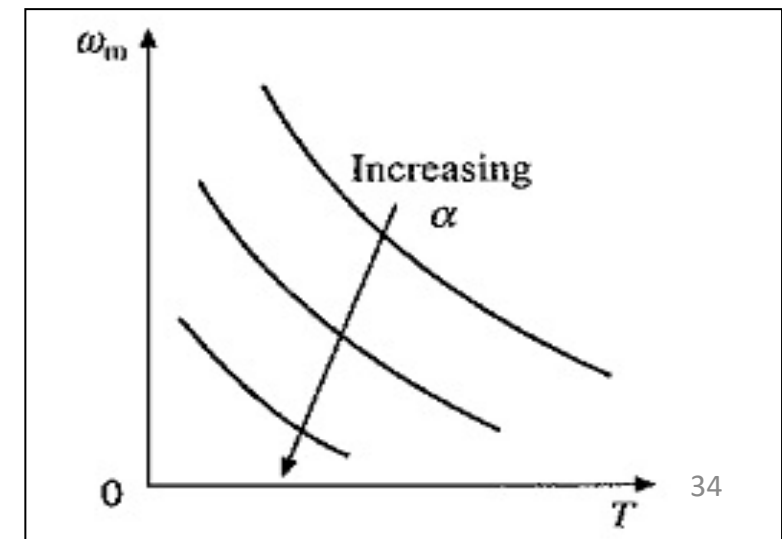- Following sequence of steps are used to calculate speed-torque characteristic for a given α taking into account non-linearity of the magnetic circuit:
- A value is chosen for I_a . Corresponding value of K_a is obtained from the magnetization characteristic of the motor.




Employing a single thyristor, is commonly used for the control of fractional hp universal, dc series and permanent-magnet dc motors. Such drives are employed in hand tools and small domestic appliances.

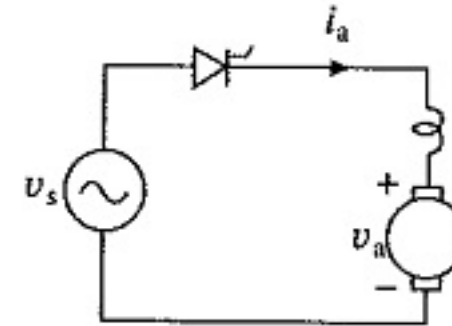
Universal motors may also be controlled by a triac ac voltage controller as shown in Fig




(a)

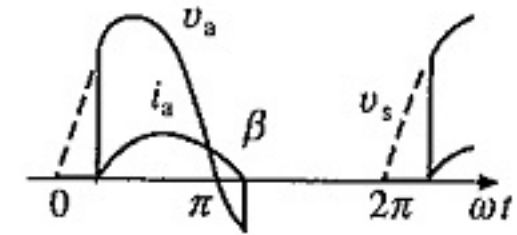

(b)

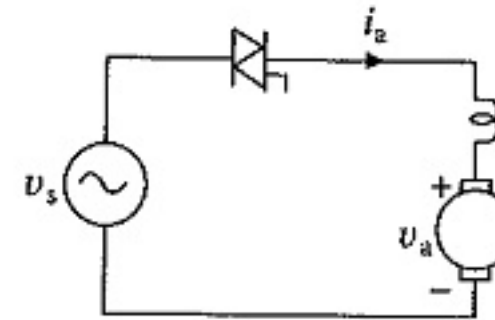

(a)

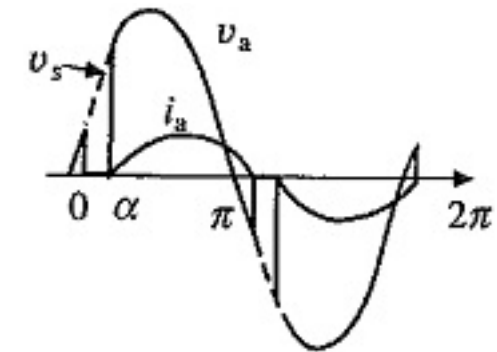

(b)

Supply harmonics, power factor and ripple in motor current

1. Distortion of Supply:

- Source current of a rectifier has harmonics. In a weak ac source, with high internal impedance, current harmonics distort source voltage.
- Source voltage and current distortions have several undesirable effects including interference with other loads connected to the source and radio frequency interference in communication equipment.

2. Low power factor

$$PF = \frac{\text{Real Power}}{\text{Apparent Power}} = \frac{VI_1 \cos \phi_1}{VI_{\text{rms}}}$$

$$PF = \frac{I_1}{I_{\text{rms}}} \cos \phi_1 = \mu \cos \phi_1$$

where

V = rms source voltage, V

I_{rms} = rms source current, A

I_1 = fundamental component of source current, A



ϕ_1 = phase difference between V and I_1 , rad

3. Ripple in Motor Current

- The rectifier output voltage is not perfect dc, but consists of harmonics in addition to dc component. Therefore motor current also has harmonics in addition to dc component.
- The presence of harmonics, makes rms and peak values of motor currents higher than average value (dc component). Since flux is constant, torque is contributed only by the average value of current. The harmonics produce fluctuating torques, the average value of which is zero.
- The presence of harmonics increases both copper loss and core loss. Hence for a allowable temperature rise, the torque and power outputs have lesser values than rated values. Due to the presence of harmonics, peak value of current increases and commutation condition deteriorates. Hence, the current that the motor can commute without sparking at the brushes has a lower dc component than the rated motor current. Thus the derating of motor occurs due to this also. On the whole the motor output (power and torque) has to be restricted considerably below rated value in order to avoid thermal overloading and sparking at brushes.

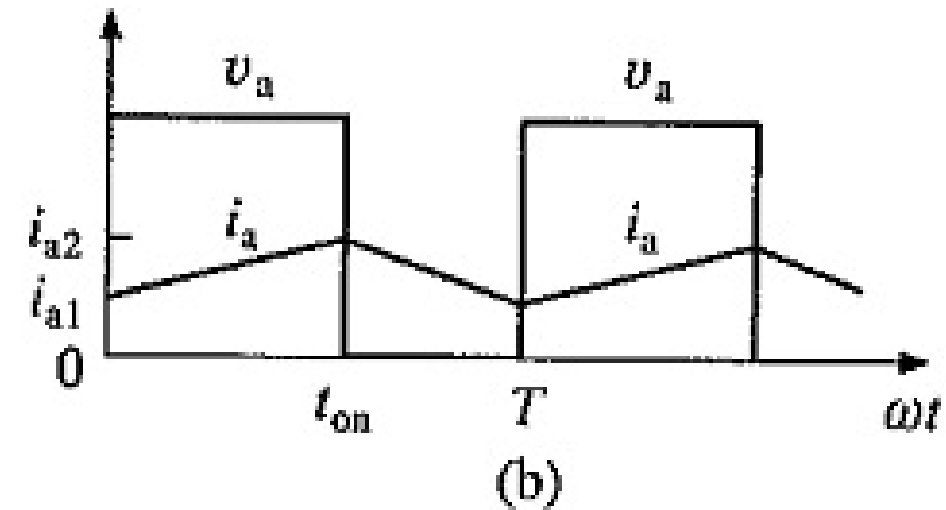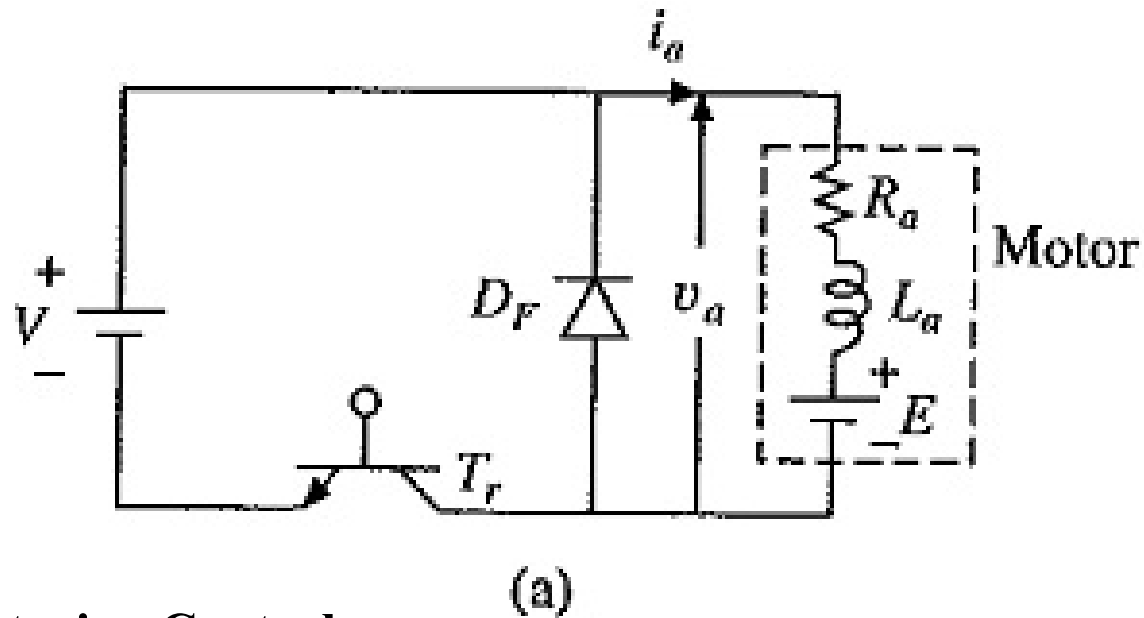7. Chopper Control of Separately Excited DC Motor

<https://www.youtube.com/watch?v=Z9jesVq4Vro>




i. Motoring Control :

- A transistor Chopper Control of Separately Excited DC Motor drive is shown in Fig. (a).
- **Transistor Tr** is operated periodically with period T and remains ON for a duration t_{on} .
- Present day choppers operate at a frequency which is high enough to ensure **continuous conduction**.
- **Waveforms** of motor terminal voltage **va** and armature current **ia** for continuous conduction are shown in Fig. (b).
- During **ON-period** of the transistor, $0 \leq t \leq t_{on}$, the motor terminal voltage is V.

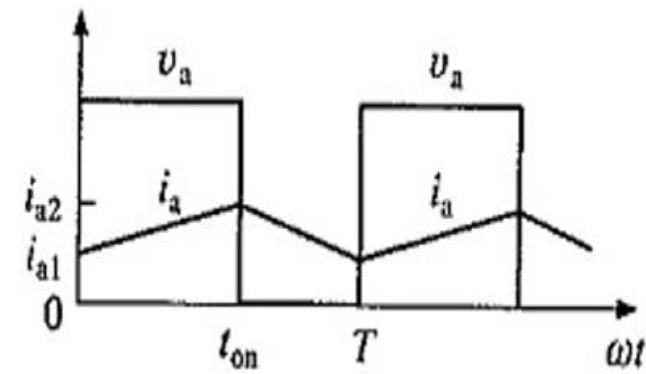i. Motoring Control cntd.

The operation is described by

$$R_a i_a + L_a \frac{di_a}{dt} + E = V, \quad 0 \leq t \leq t_{on}$$



- In this interval, **armature current increases** from i_{a1} to i_{a2} . Since motor is connected to the source during this interval, it is called **Duty Interval**.
- At $t = t_{on}$, T_r is turned-off. Motor current **freewheels** through diode D_F and motor terminal voltage is zero during interval $t_{on} \leq t \leq T$.
- Motor operation during this interval, known as **freewheeling interval**, is described by $R_a i_a + L_a \frac{di_a}{dt} + E = 0, \quad t_{on} \leq t \leq T$
- Motor **current decreases** from i_{a2} to i_{a1} during this interval.
- Ratio of duty interval t_{on} to chopper period T is called **duty ratio or duty cycle (δ)**. Thus

$$\delta = \frac{\text{Duty interval}}{T} = \frac{t_{on}}{T}$$

$$I_a = \frac{\delta V - E}{R_a}$$




$$V_a = \frac{1}{T} \int_0^{t_{on}} V dt = \delta V$$

$$\omega_m = \frac{\delta V}{K} - \frac{R_a}{K^2} T$$

$$\begin{aligned} V_a &= E + I_a R_a \\ \delta V &= E + I_a R_a \\ I_a R_a &= \delta V - E \\ I_a &= \frac{\delta V - E}{R_a} \end{aligned}$$

- The nature of speed torque characteristic is shown in Fig

ii. Regenerative Braking:

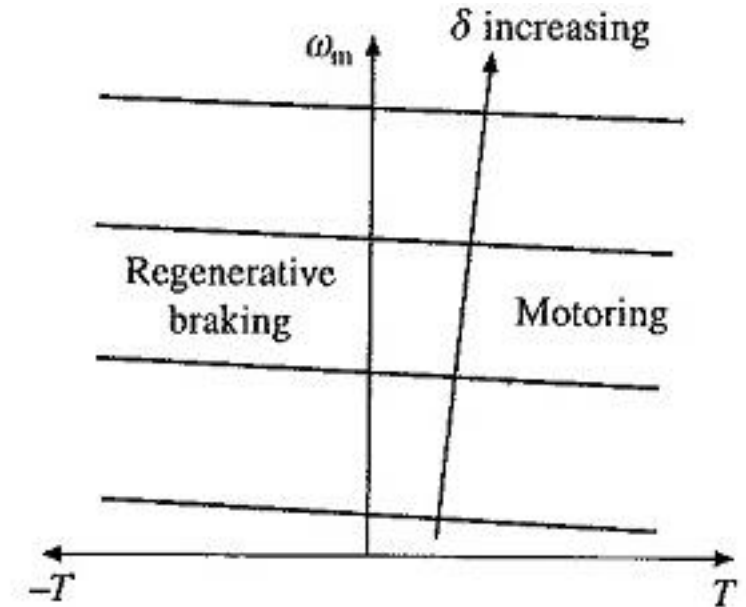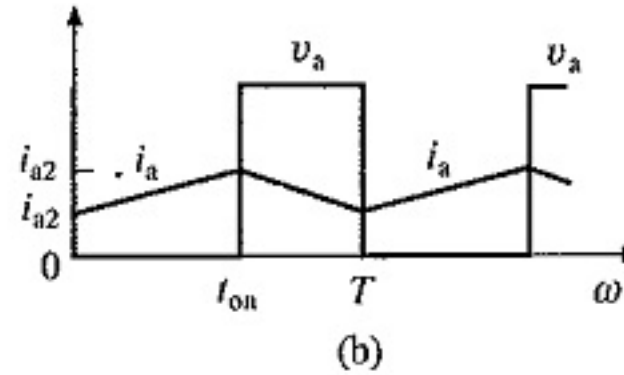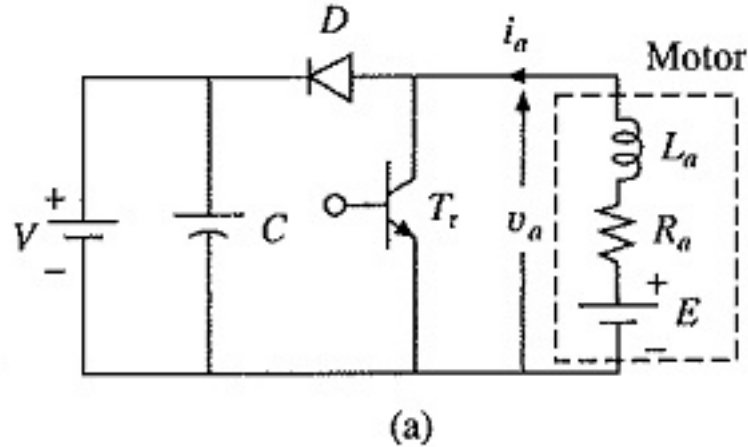

- Chopper Control of Separately Excited DC Motor for regenerative braking operation is shown in Fig. (a).
- Transistor T_r** is operated periodically with a period T and ON-period of t_{on} .
- Waveforms** of motor terminal voltage v_a and armature current i_a for continuous conduction.
- Usually an external inductance is added to increase the value of L_a .
- When **T_r is ON**, i_a increase from **i_{a1} to i_{a2}** .

- If δ is again defined as the ratio of duty interval to period T , then

$$\delta = \frac{\text{Duty interval}}{T} = \frac{T - t_{\text{on}}}{T}$$

$$V_a = \frac{1}{T} \int_{t_{\text{on}}}^T V dt = \delta V$$

$$I_a = \frac{E - \delta V}{R_a}$$


Since I_a has reversed

$$T = -KI_a$$

$$\omega_m = \frac{\delta V}{K} - \frac{R_a}{K^2} T$$



$$\begin{aligned} V_a &= E - I_a R_a \\ I_a R_a &= E - V_a \\ I_a &= \frac{E - V_a}{R_a} \end{aligned}$$

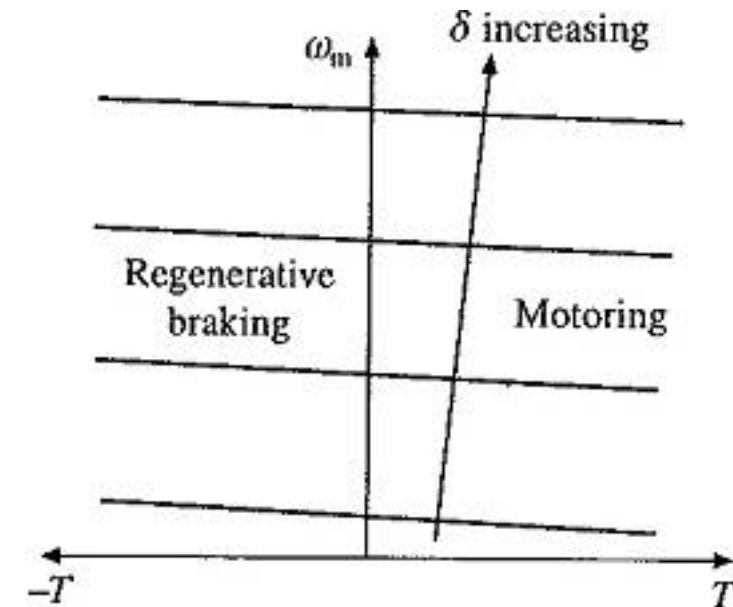The nature of speed torque characteristic is shown in Fig



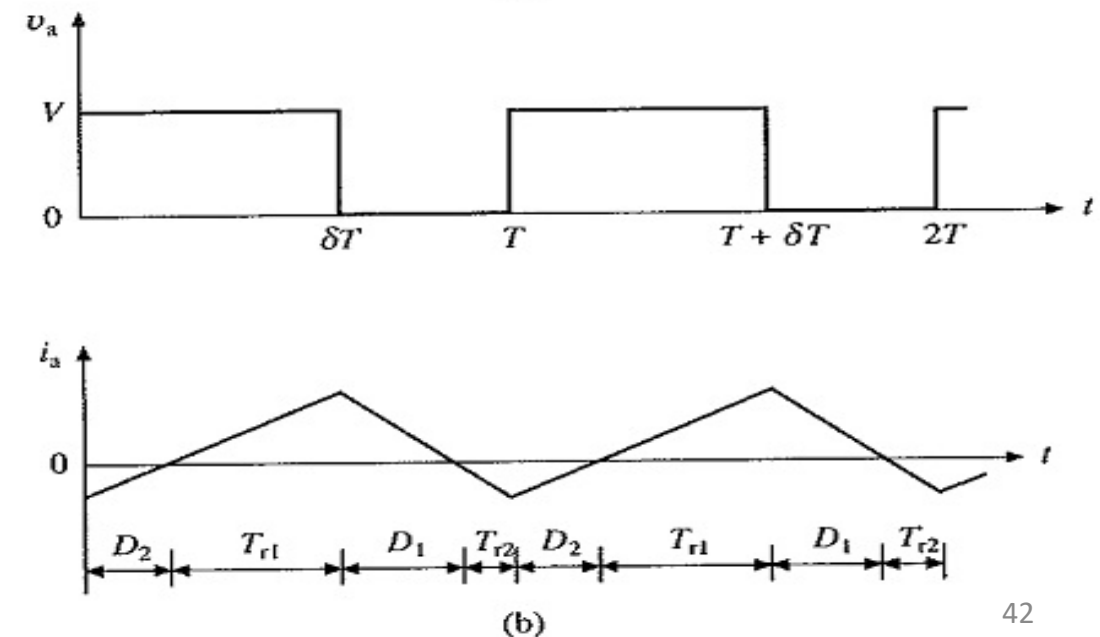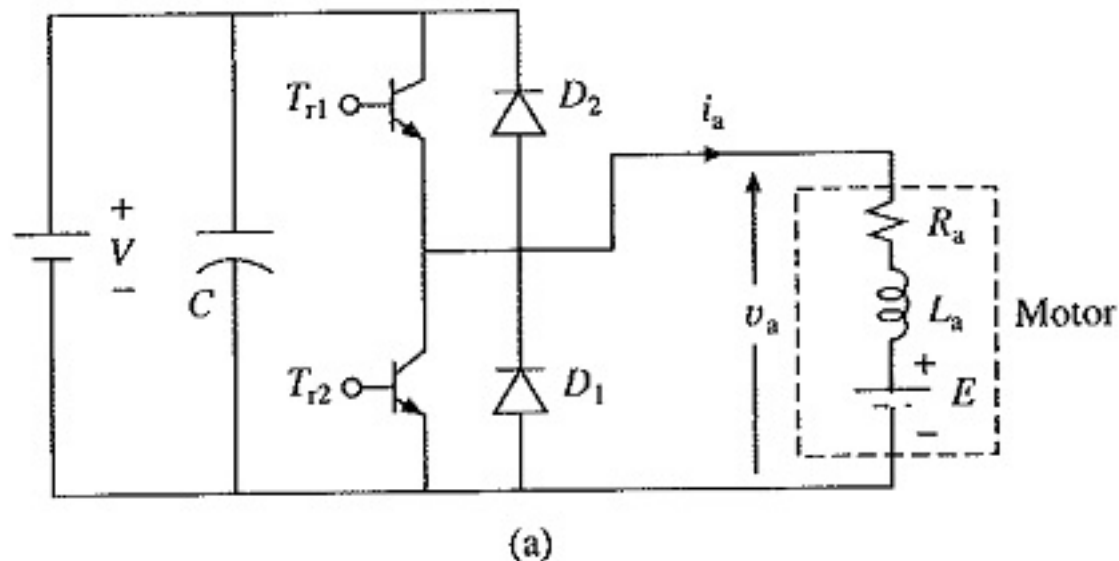iii. Motoring and Regenerative Braking

- In servo drives where fast transition from motoring to braking and vice versa is required, both T_{r1} and T_{r2} are controlled simultaneously.
- In a period T , T_{r1} is given **gate** drive from **0 to δT** and T_{r2} is given **gate** drive from **δT to T** , where δ is the duty ratio for T_{r1} . Therefore, from **0 to δT** motor is connected to source either through T_{r1} or D_2 depending on whether the motor current i_a is positive or negative.
- Since $V > E$, during this period the **rate of change of current** is always **positive**.
- Similarly from **δT to T** , motor armature is shorted either through D_1 or T_{r2} depending on whether i_a is positive or negative and during this period **rate of change of current** is always **negative**.





$$V_a = \delta V$$

$$I_a = \frac{\delta V - E}{R_a}$$



- Above equation suggests that motoring operation (+ve I_a) takes place when $\delta > (E/V)$ and regenerative braking operation takes place when $\delta < (E/V)$ and transition from motoring to braking and vice versa occurs when $\delta = (E/V)$.
- The above equations are similar to those obtained for chopper of Fig. (5.41), and therefore, given the same numbers.

Dynamic Braking:

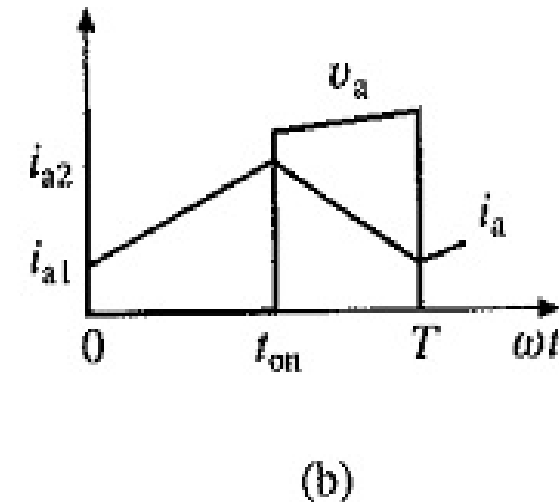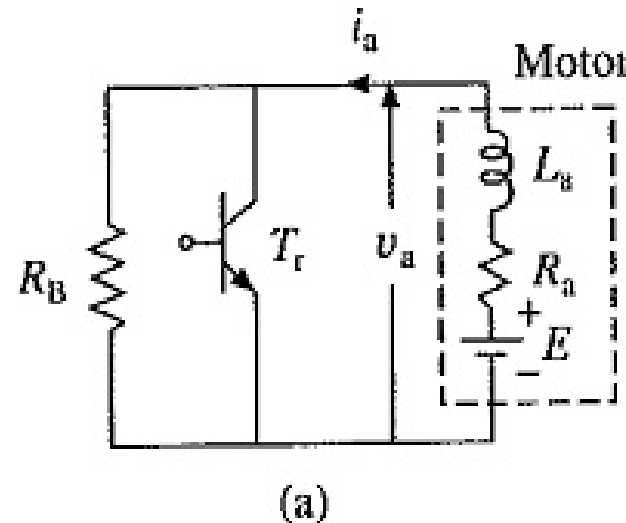- Dynamic braking circuit and its waveforms are shown in Fig.
- During the interval $0 \leq t \leq t_{on}$, i_a increases from i_{a1} to i_{a2} . A part of generated energy is stored in inductance and rest is dissipated in R_a and T_r . During interval $t_{on} \leq t \leq T$, i_a decreases from i_{a2} to i_{a1} .



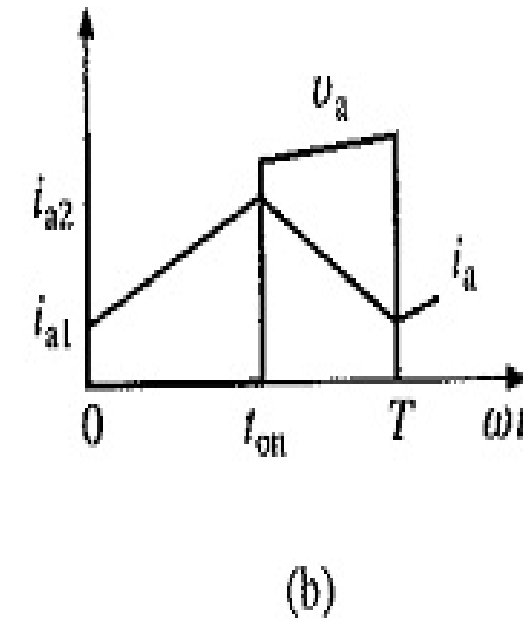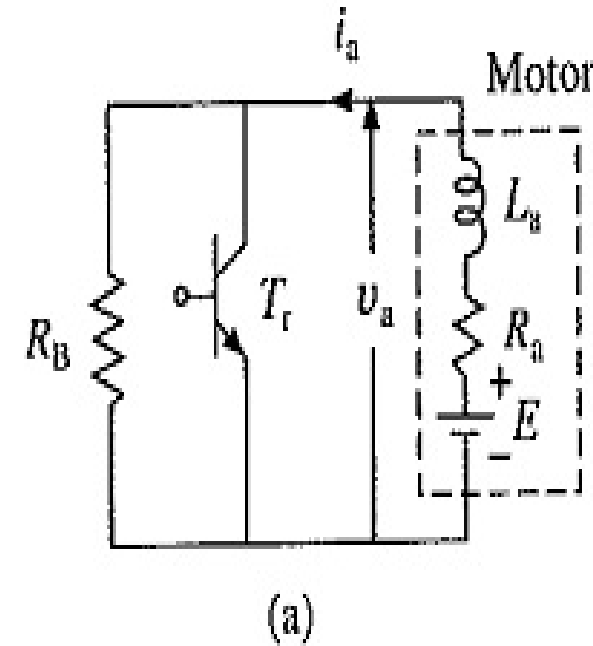
- The energies generated and stored in inductance are dissipated in braking resistance R_B , R_a .
- Transistor T_r controls the magnitude of energy dissipated in R_B , and therefore, controls its effective value.
- If i_a is assumed to be rippleless dc, then energy consumed E_N by R_B during a cycle of chopper operation is




$$E_N = I_a^2 R_B (T - t_{on}) \quad \left| \quad P = \frac{E_N}{T} = I_a^2 R_B (1 - \delta) \quad R_{BE} = \frac{P}{I_a^2} = R_B (1 - \delta) \quad \delta = \frac{t_{on}}{T} \right.$$

Chopper Control of Series Motor:

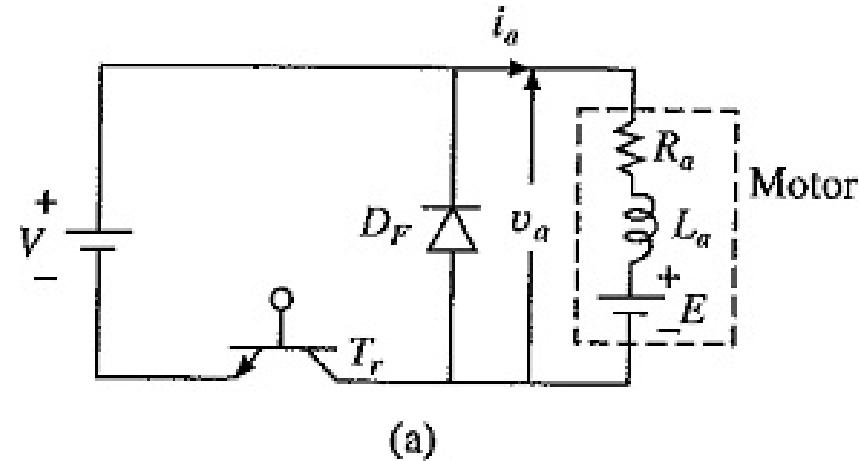
- Motoring** : Chopper Control of Series Motor and **va and ia waveforms** will be same as shown in Fig. V_a is given by Eq.


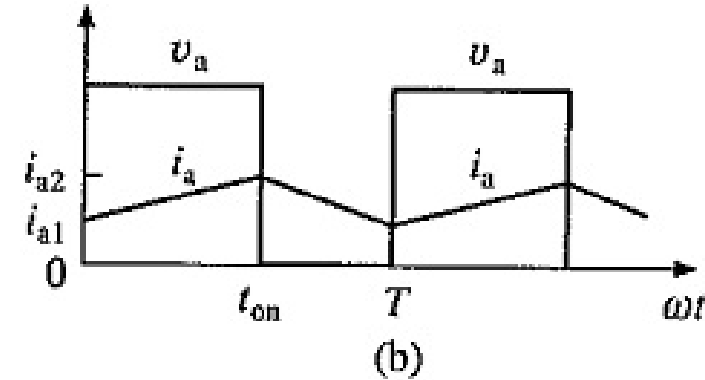
$$V_a = \frac{1}{T} \int_0^{t_{on}} V dt = \delta V$$





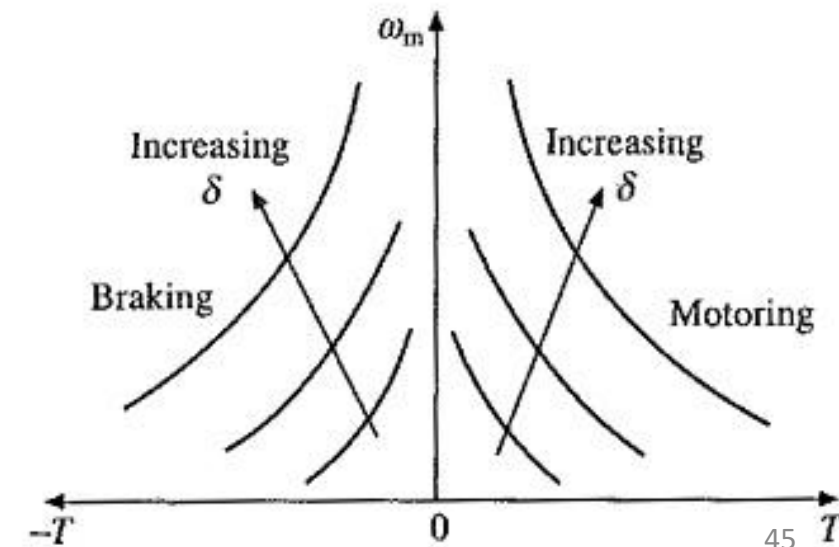- However, e is not constant but varies with i_a . Due to saturation of magnetic circuit, relationship between e and i_a is non-linear.
- The approximation is already described and is applicable here.
- Consequently, motor performance can be calculated. The nature of speed torque curves is shown in Fig.



Regenerative braking

- With Chopper Control of Series Motor, regenerative braking of series motor can also be obtained. Power circuit of Fig.(a) is employed.
- During regenerative braking, series motor **functions as a self-excited series generator**. For self-excitation, current flowing through field winding should assist residual magnetism.
- Therefore, when **changing from motoring to braking connection**, while **direction of armature current should reverse**, **field current should flow in the same direction**.
- This is achieved by reversing the field with respect to armature when changing from motoring to braking operation. Waveforms of v_a and i_a will be same as those of Fig.(b).
- For a chosen value of I_a , K_a is obtained from magnetization characteristic. Then T and ω_m are obtained from Eqs., respectively.
- The nature of speed-torque characteristics is shown in Fig.. Such characteristics give unstable operation with most [loads](#). Consequently, regenerative braking of the series motor is difficult.

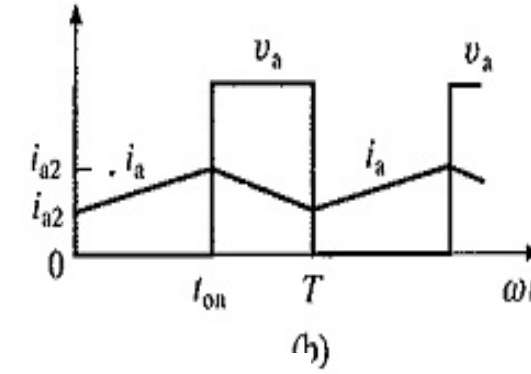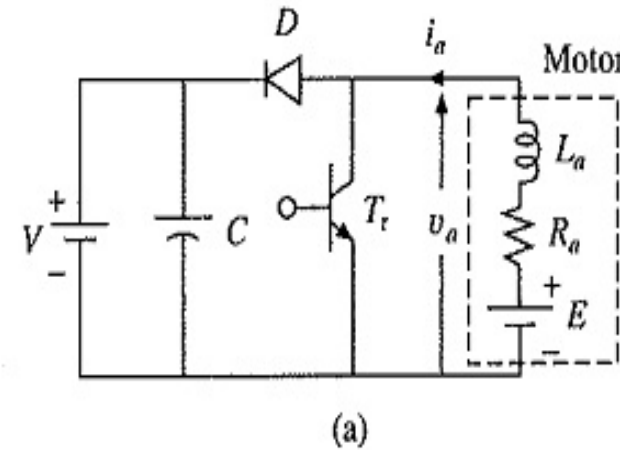

$$\omega_m = \frac{\delta V + I_a R_a}{K_a}$$


$$T = -K_a I_a$$

Numericals

- Refer Notes-For Numericals solved in the class

Closed Loop Speed Control of DC Motor

- The drive employs inner current control loop and outer speed loop.
- Such a drive will operate at a constant field current and variable armature voltage below the base speed, and at a constant armature voltage and variable field current above the base speed.
- Both armature and field, are therefore, fed from fully-controlled rectifiers.
- Since, the armature is fed from a fully-controlled rectifier, forward braking is not possible; the drive will decelerate due to load torque only.
- Because of inner current control with current limiter, the acceleration will take place at the maximum permissible current and torque.

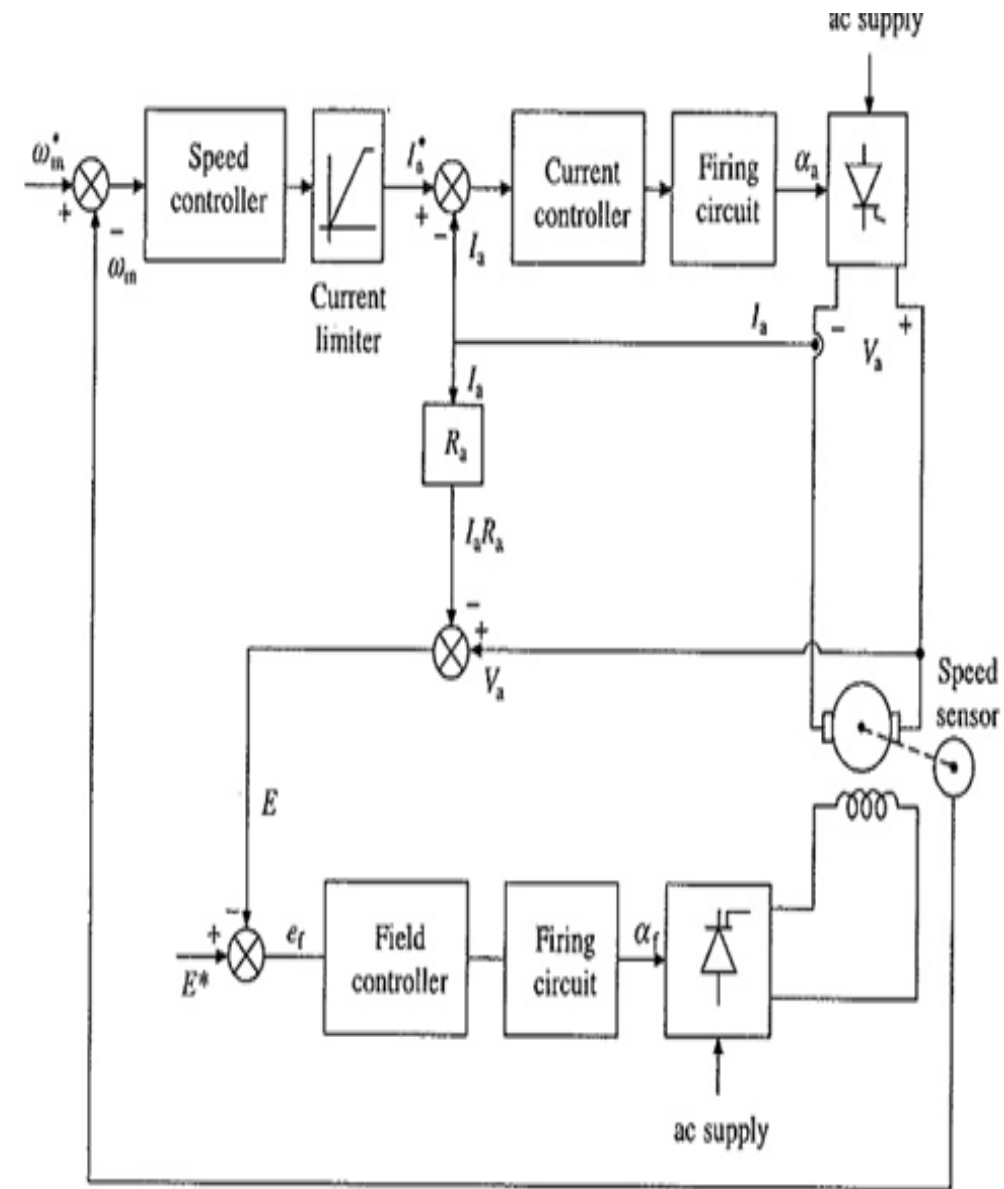

- In semiconductor converter fed drives PI (proportional and integral) controller is often used because it filters out noise which can otherwise become a problem.
- PI controller also gives good steady-state accuracy.
- Let us first examine the operation below the base speed. In the field control loop, the back emf E is compared with a reference voltage E^* which is chosen to be between 0.85 to 0.95 of the rated armature voltage.
- The higher value is used for motors with low armature circuit resistance.
- For speeds below base speed, the field controller saturates due to large value of error e_f .
- The firing angle of field rectifier α_f is maintained at zero, applying rated voltage to the field.
- This ensures rated field current for motor operation below base speed (ω_{mb}).
- When speed reference is increased from ω^*_{m1} to ω^*_{m2} ($\omega^*_{m2} < \omega_{m1}$) due to large speed error, the current limiter saturates and sets the current reference at the maximum permissible value.